

9. 时序电路分析



xgsun@fudan.edu.cn

孙晓光


2024-10-27



1

时序电路分析


时序逻辑电路 的 基本结构

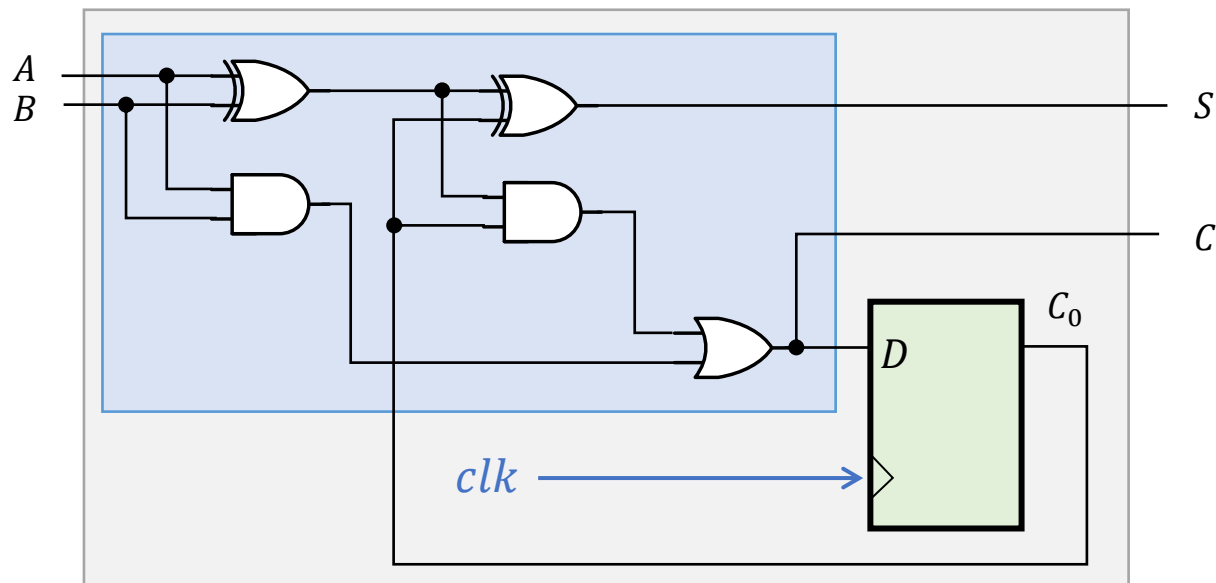

	0	1	1	0
+	0	0	1	1
<hr/>				
	1	0	0	1
	0	1	1	0



每个时钟，从低位开始逐位开始计算

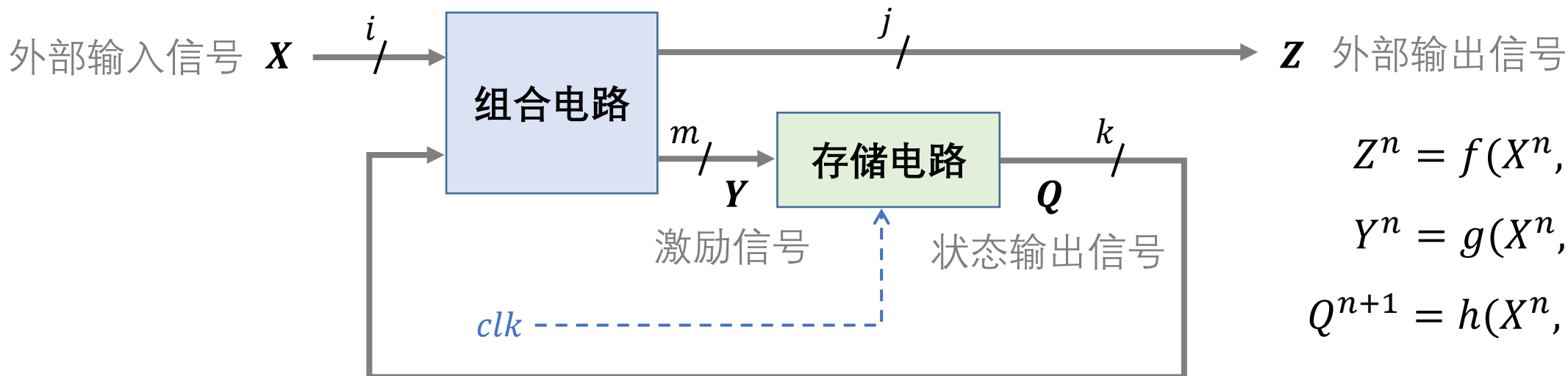


$$Z^n = f(X^n, Q^n) \text{ 输出方程}$$

$$Y^n = g(X^n, Q^n) \text{ 激励方程}$$


$$Q^{n+1} = h(X^n, Q^n) \text{ 状态方程}$$

组合电路、时序电路

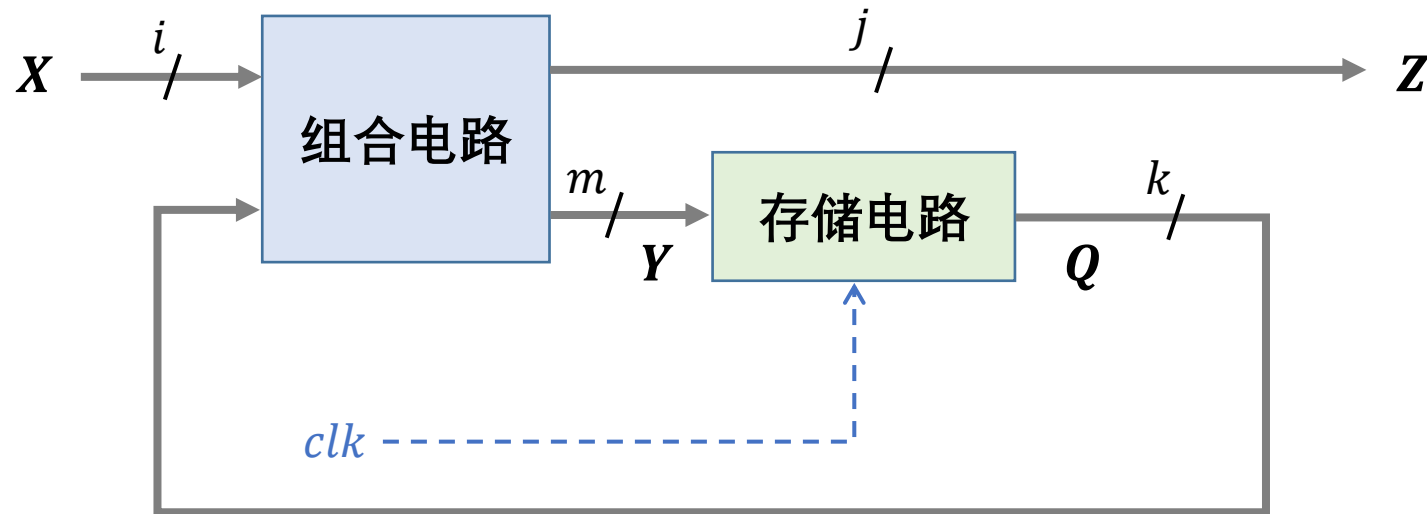- **组合逻辑电路**：任一时刻的**输出**仅与该时刻**输入**变量的取值有关，而与输入变量的历史情况无关。
- **时序逻辑电路**：任一时刻的**输出**不仅与该时刻**输入**变量的取值有关，而且与电路的**原状态**，即过去的输入情况有关。



时序逻辑电路分析

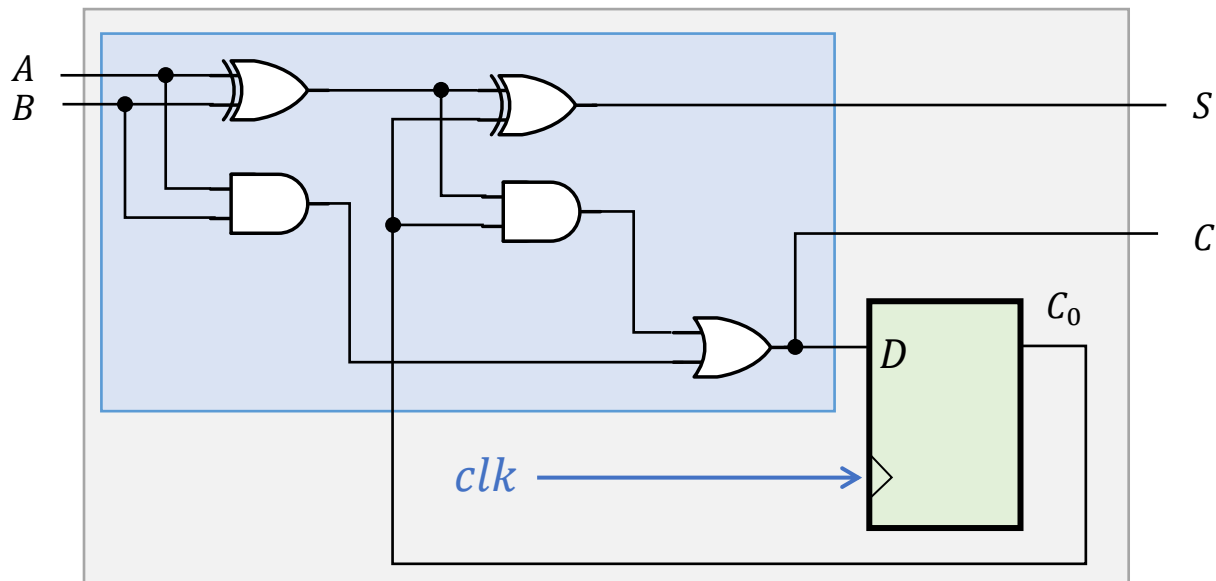

输出方程: $S = A \oplus B \oplus C_0$


激励方程: $C = (A \oplus B) C_0 + AB$

状态方程: $C_0^{n+1} = C$ $Q^{n+1} = D$



$= (A \oplus B) C_0 + AB$

	0	1	1	0	A
+	0	0	1	1	B
<hr/>					
	1	0	0	1	S
	0	1	1	0	C

看clk上升沿之前

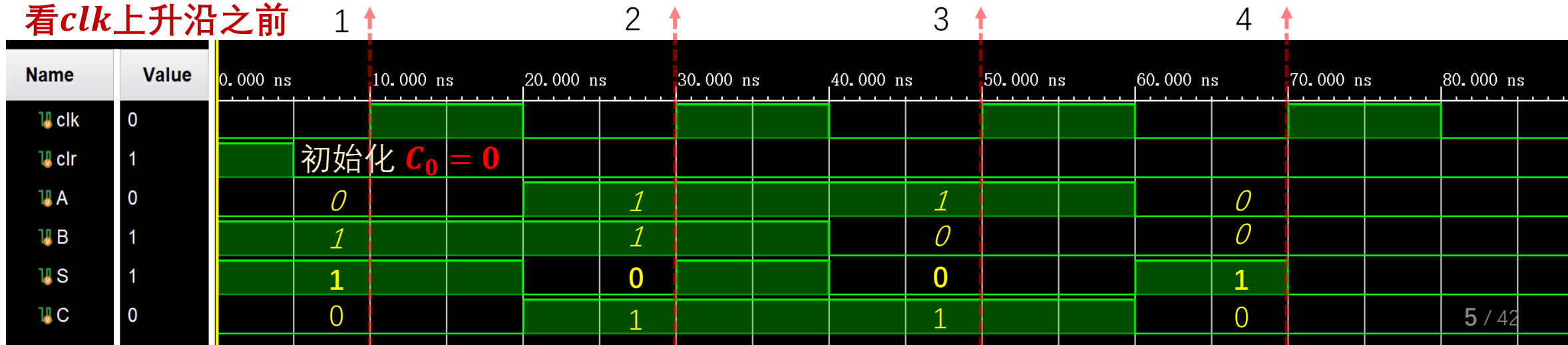


时序逻辑电路 的 通用结构

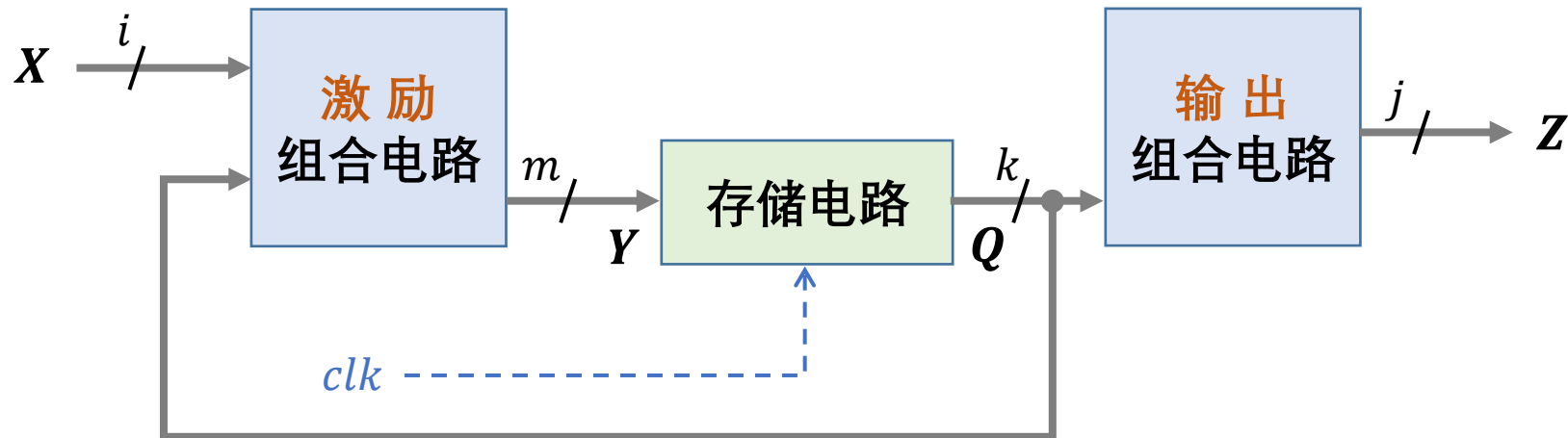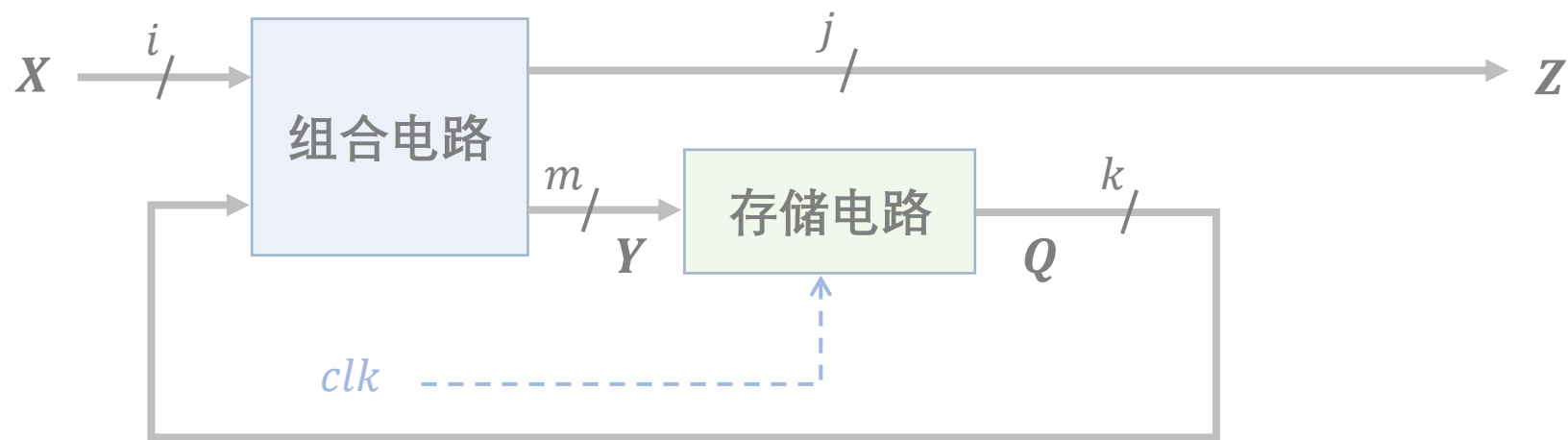


从输出Z看...

Mealy

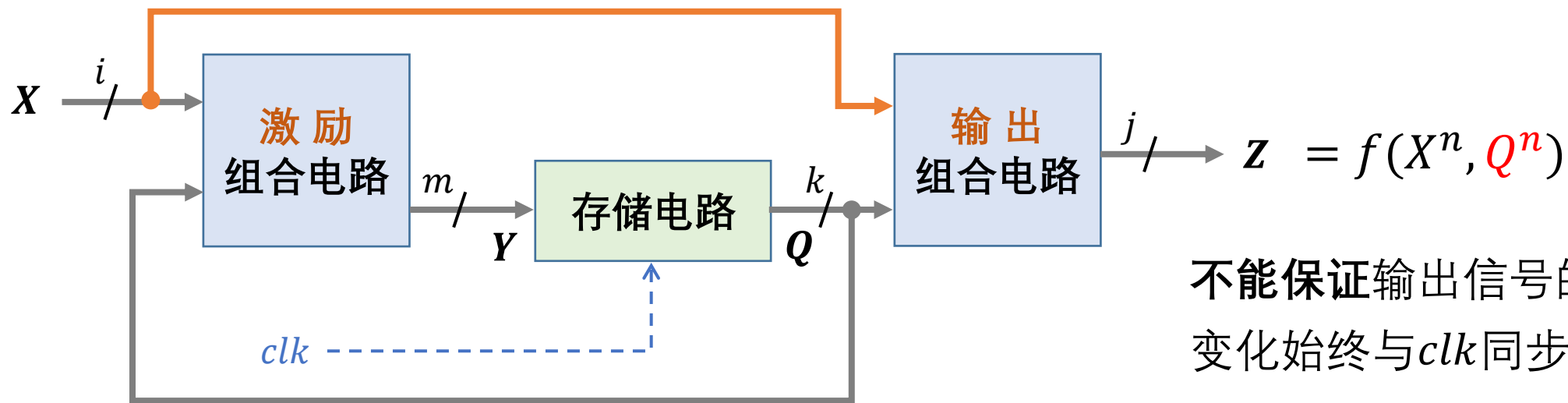


不能保证输出信号的变化始终与 clk 同步.

Moore

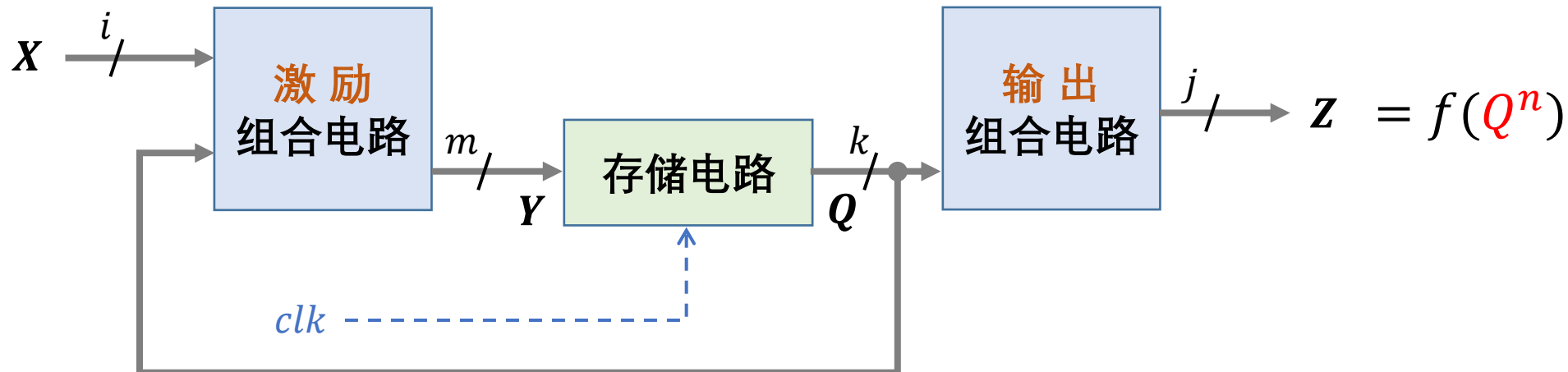


Mealy 变 Moore


Mealy

 

Moore

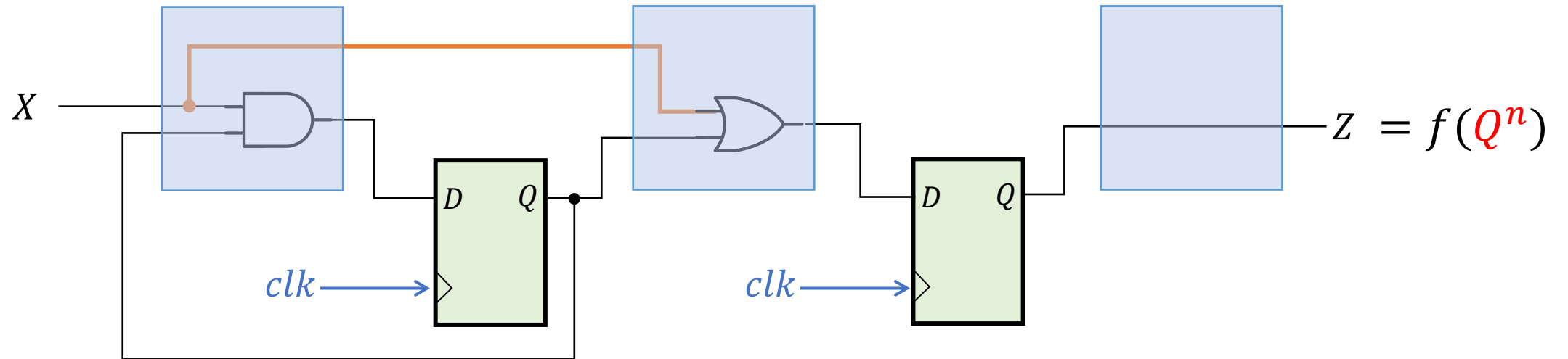

【例1】同步时序电路分析

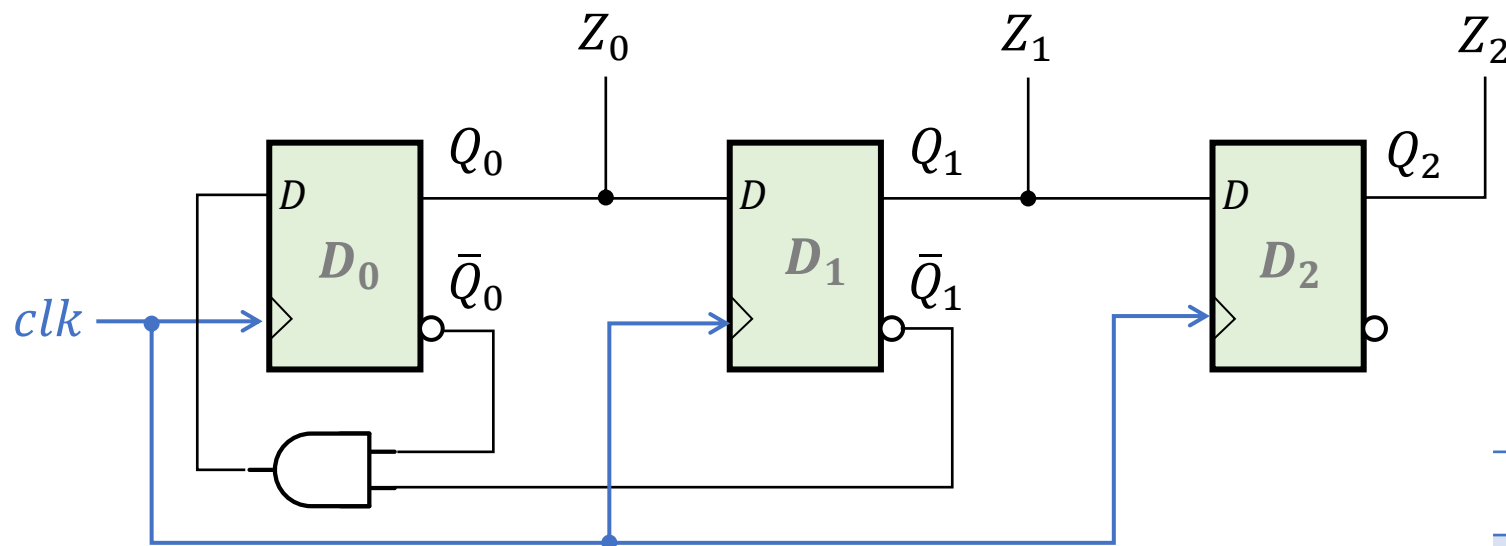

激励方程: $D_2 = Q_1$, $D_1 = Q_0$, $D_0 = \bar{Q}_1 \bar{Q}_0$

Moore

特征方程: $Q^* = D$


没有输入

状态方程: $Q_2^* = Q_1$, $Q_1^* = Q_0$, $Q_0^* = \bar{Q}_1 \bar{Q}_0$

输出方程: $Z_2 = Q_2$, $Z_1 = Q_1$, $Z_0 = Q_0$


$Q_2 Q_1 Q_0$	$Q_2^* Q_1^* Q_0^*$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	1 0 0
0 1 1	1 1 0
1 0 0	0 0 1
1 0 1	0 1 0
1 1 0	1 0 0
1 1 1	1 1 0

【例1】同步时序电路分析

 



自启动电路

如果电路处于任何一个无效状态，经过若干时钟脉冲后，都可以自动进入有效状态的电路。

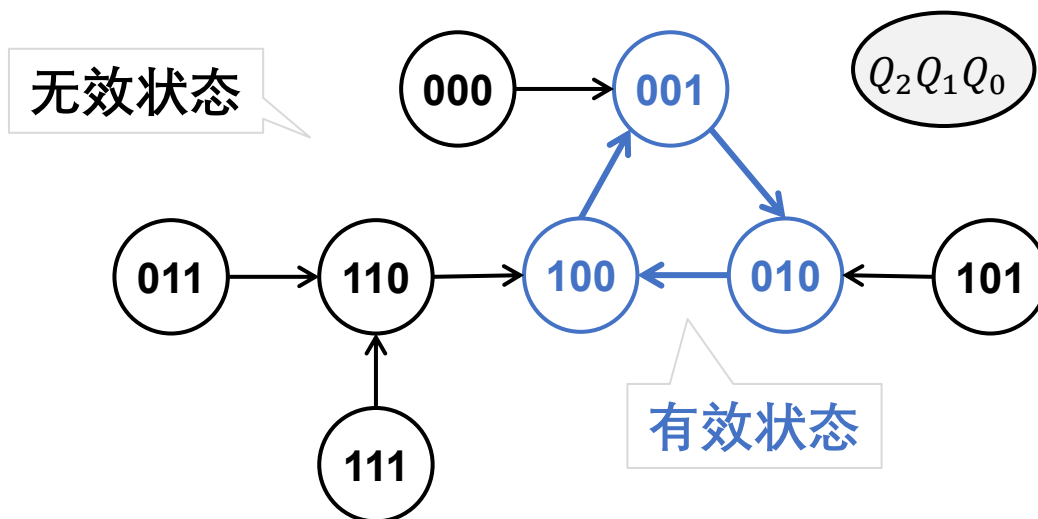

$Q_2 Q_1 Q_0$	$Q_2^* Q_1^* Q_0^*$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	1 0 0
0 1 1	1 1 0
1 0 0	0 0 1
1 0 1	0 1 0
1 1 0	1 0 0
1 1 1	1 1 0



【例1】同步时序电路分析

 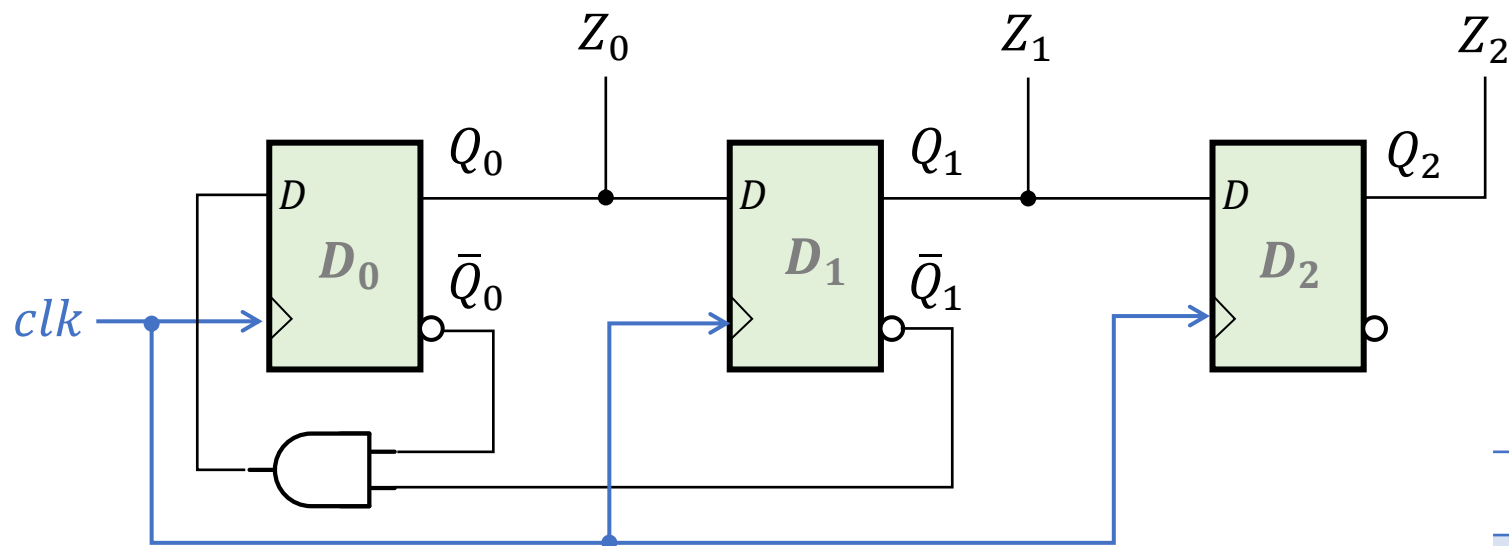


$Q_2 Q_1 Q_0$	$Q_2^* Q_1^* Q_0^*$
0 0 0	0 0 1
0 0 1	0 1 0
0 1 0	1 0 0
0 1 1	1 1 0
1 0 0	0 0 1
1 0 1	0 1 0
1 1 0	1 0 0
1 1 1	1 1 0

【练习1】 状态表 => 状态图

S	S^*/Z	
	$A = 0$	$A = 1$
a	$d / \mathbf{1}$	$b / \mathbf{0}$
b	$d / \mathbf{1}$	$c / \mathbf{0}$
c	$d / \mathbf{1}$	$a / \mathbf{0}$
d	$b / \mathbf{1}$	$c / \mathbf{0}$

  

【例2】JK触发器电路分析：公式法

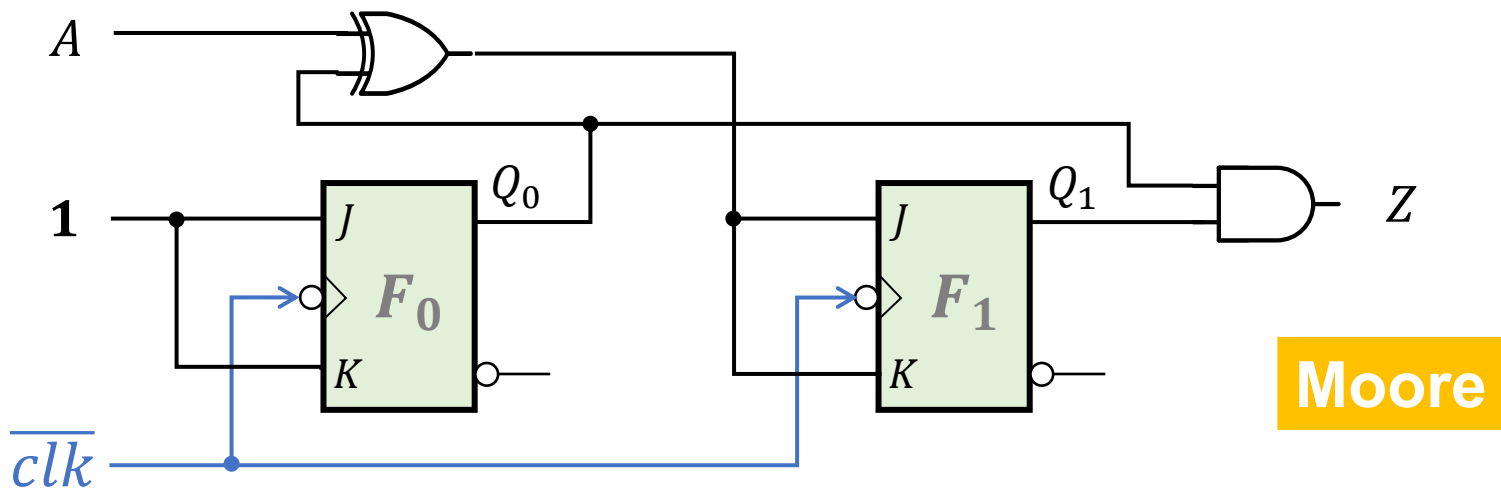

Q_1Q_0	$Q_1^*Q_0^*$		Z
	$A = 0$	$A = 1$	
0 0	0 1	1 1	0
0 1	1 0	0 0	0
1 0	1 1	0 1	0
1 1	0 0	1 0	1

激励方程： $J_0 = K_0 = 1$

$J_1 = K_1 = A \oplus Q_0$

特征方程： $Q^* = J\bar{Q} + \bar{K}Q$


状态方程： $Q_0^* = J_0\bar{Q}_0 + \bar{K}_0Q_0 = \bar{Q}_0$, $Q_1^* = J_1\bar{Q}_1 + \bar{K}_1Q_1$

输出方程： $Z = Q_1Q_0$


$A = 0$ 时，递增计数
 $A = 1$ 时，递减计数

$$= (A \oplus Q_0)\bar{Q}_1 + \overline{A \oplus Q_0}Q_1$$

$$= A \oplus Q_0 \oplus Q_1$$

 

【例2】JK触发器电路分析：特征表法

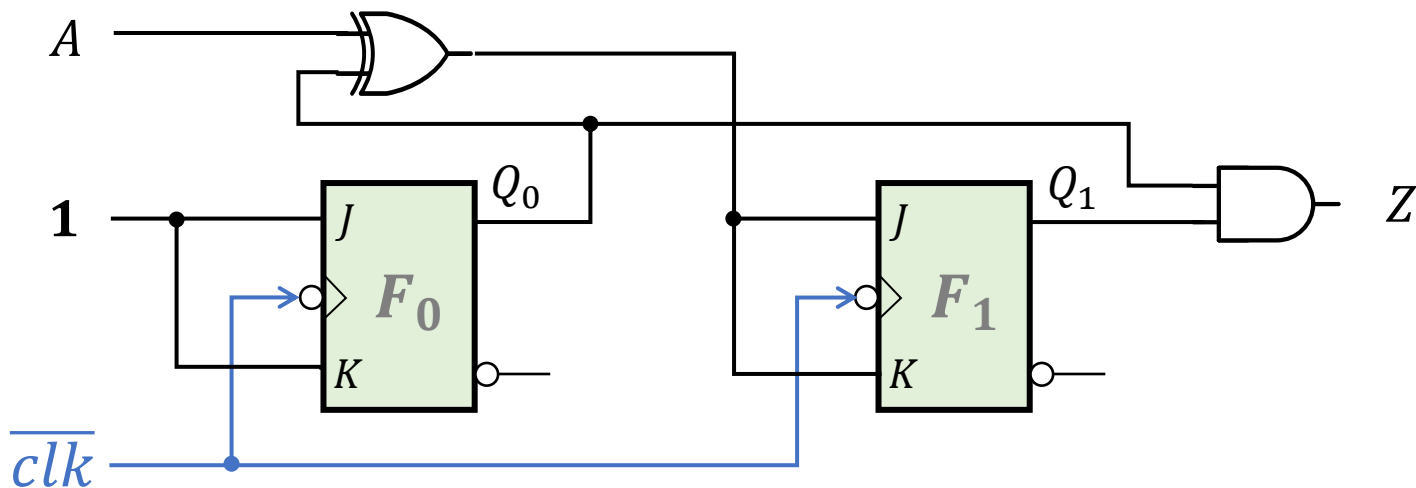

激励方程： $J_0 = K_0 = 1$


$J_1 = K_1 = A \oplus Q_0$

输出方程： $Z = Q_1 Q_0$


特征表

J	K	Q^*	说明
0	0	Q	保持
1	0	1	置 1
0	1	0	置 0
1	1	\bar{Q}	翻转

$Q_1 Q_0$	$Q_1^* Q_0^*$		Z
	$A = 0$	$A = 1$	
0 0	0 1	1 1	0
0 1	1 0	0 0	0
1 0	1 1	0 1	0
1 1	0 0	1 0	1

 

【例3】T触发器电路分析

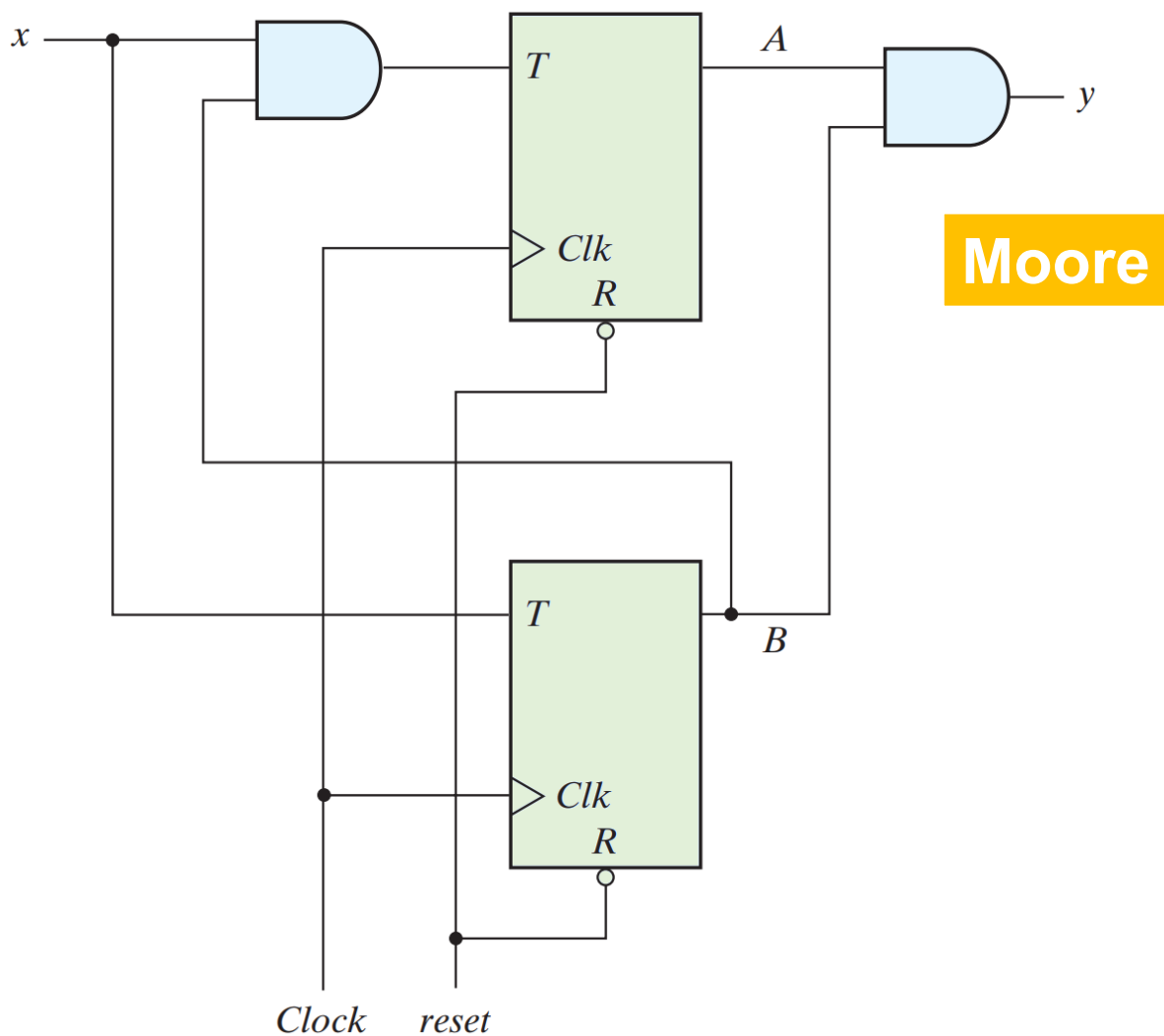


激励方程: $T_A = Bx$ $T_B = x$

特征方程: $Q^* = T \oplus Q$

状态方程: $A^* = T_A \oplus A = Bx \oplus A$

$$B^* = T_B \oplus B = x \oplus B$$


输出方程: $y = AB$

 


时序电路分析步骤

(对同步、异步时序电路都适用)

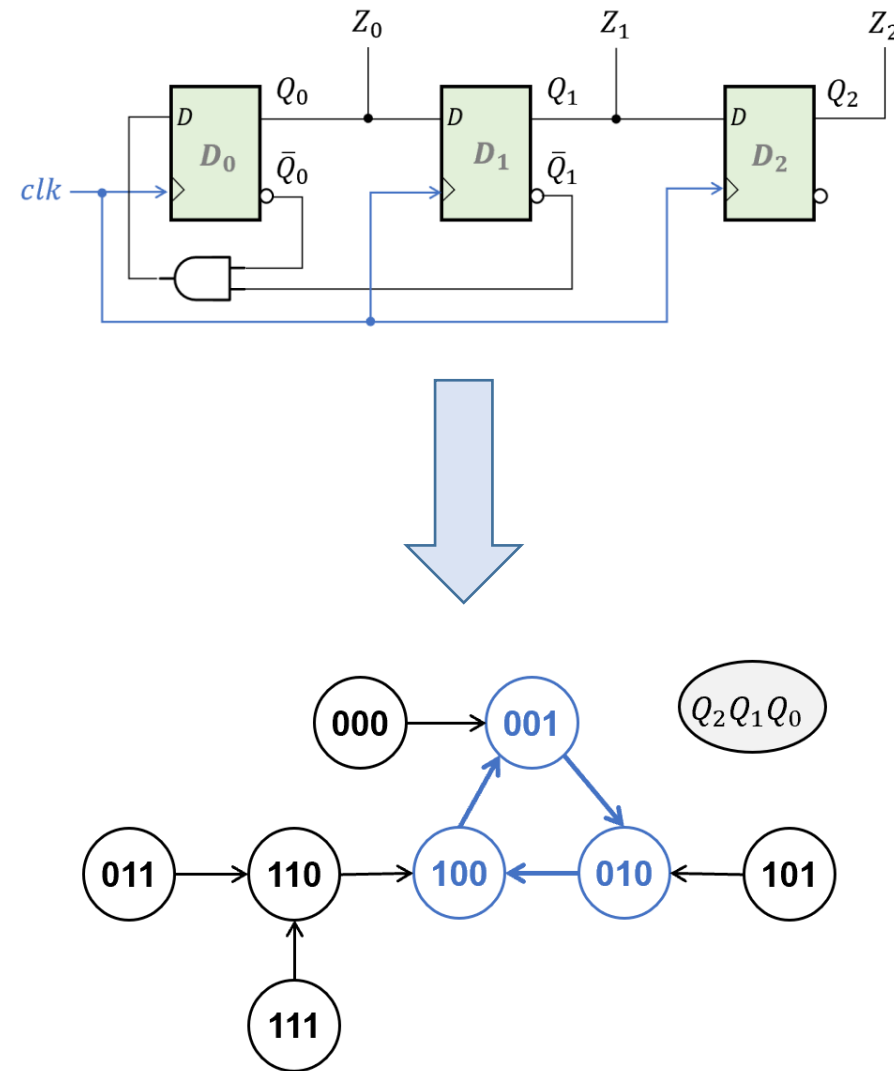- ① 分析**电路组成** (组合? 时序? Moore? Mealy?)
- ② 写出**激励方程**、**输出方程**
- ③ 写出**状态方程** / **特征表**
- ④ 画出**状态表**、**状态图**、**(波形图)**
- ⑤ 分析**输出序列**、**输入序列**的关系,
说明时序电路的逻辑功能。
- ⑥ 评估、改进电路



【例4】异步时序电路分析*

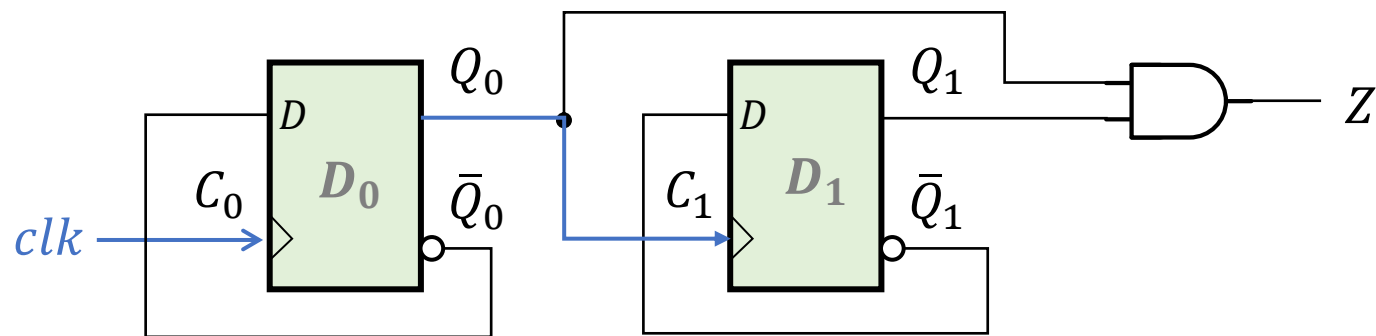

时钟方程: $C_0 = clk \uparrow$, $C_1 = Q_0 \uparrow$ 即 Q_0 由0变1

激励方程: $D_0 = \bar{Q}_0$, $D_1 = \bar{Q}_1$


特征方程: $Q^* = D$

上升沿才能转换状态,
其余时间保持原态。

状态方程: $Q_0^* = D_0 C_0 + Q_0 \bar{C}_0$ $Q_1^* = D_1 C_1 + Q_1 \bar{C}_1$
 $= \bar{Q}_0 \uparrow + Q_0 \downarrow$ $= \bar{Q}_1 \uparrow + Q_1 \downarrow$

输出方程: $Z = Q_1 Q_0$

因两个D触发器状态翻转存在延迟,
故电路存在短暂的不确定状态。

 


Q_1	Q_0	C_1	C_0	Q_1^*	Q_0^*	Z
0	0	\uparrow	\uparrow	1	1	0
0	1	\downarrow	\uparrow	0	0	0
1	0	\uparrow	\uparrow	0	1	0
1	1	\downarrow	\uparrow	1	0	1

同步时序电路、异步时序电路

时序电路


- 同步时序电路：各个触发器的时钟脉冲相同。一般用触发器实现。

在非时钟有效沿期间，触发器处于保持状态。

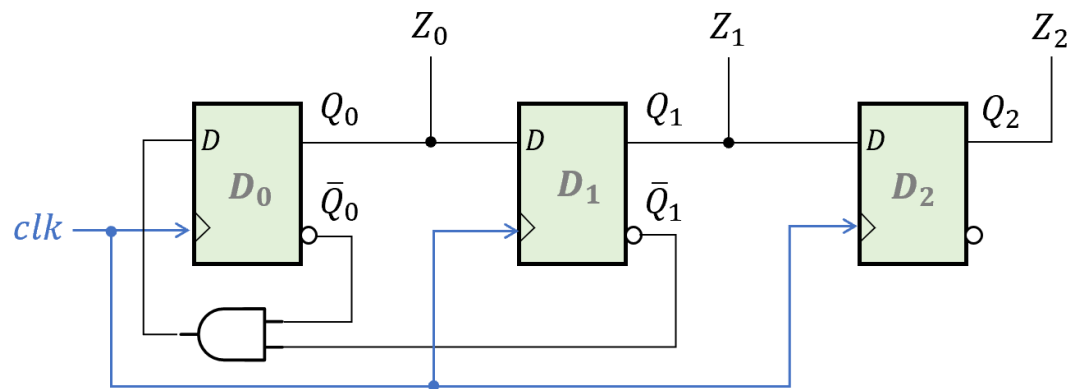


- 异步时序电路：各个触发器的时钟脉冲不同。既可用触发器、也可用锁存器。

电路状态的翻转有先有后。

 


同步时序逻辑电路中的时钟偏移

从同一时钟源出发的时钟脉冲，通过不同路径到达每个触发器的时间不同而产生的偏差。

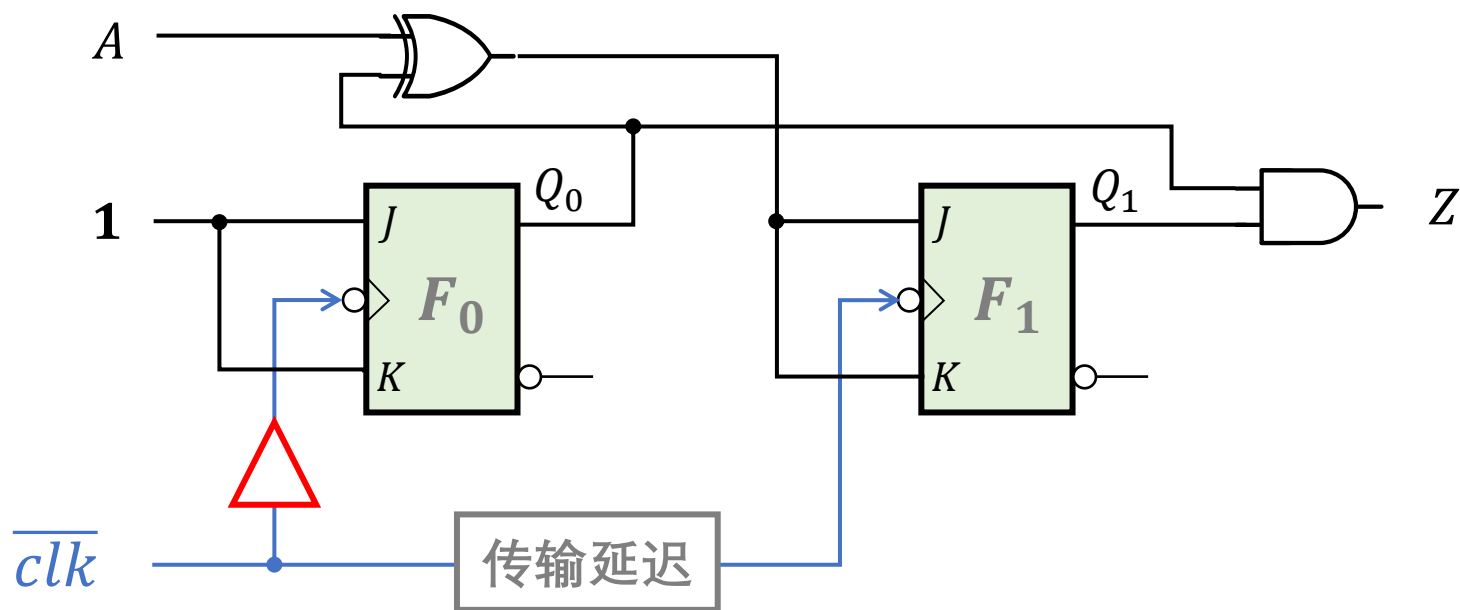

解决方法：增加缓冲器、对称布局……

【例5】电路分析

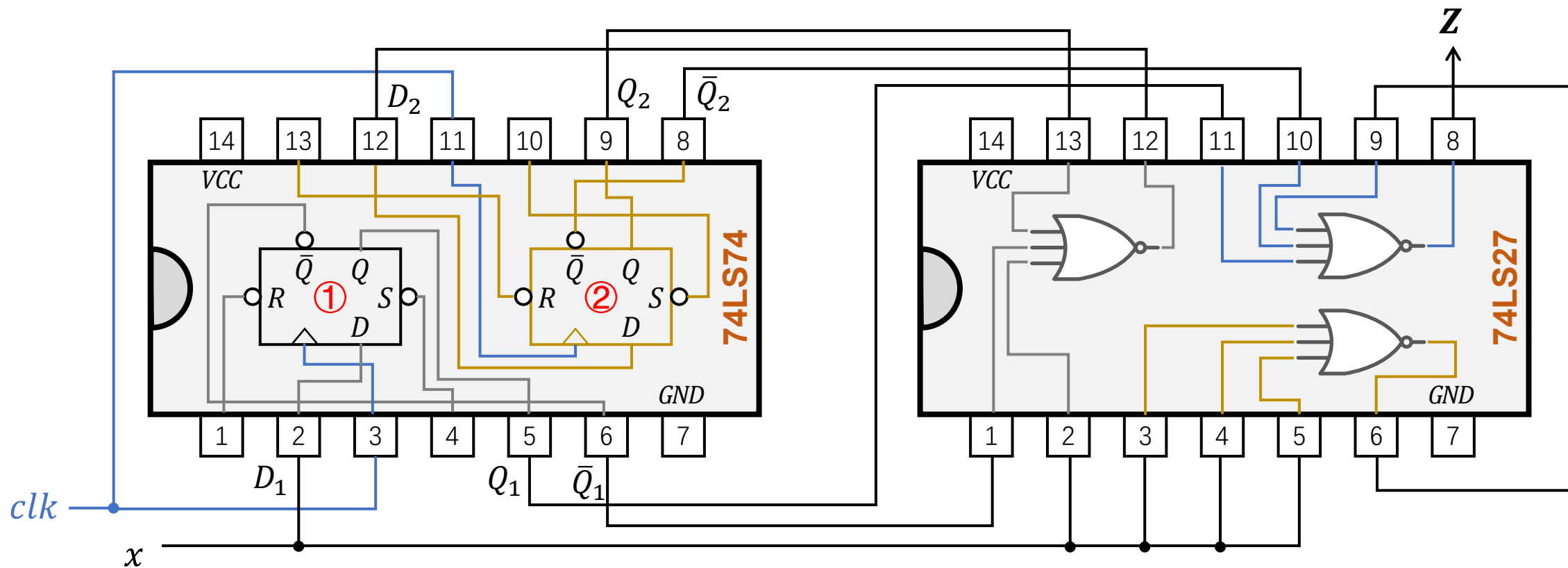


$$Z = \overline{\bar{x} + \bar{Q}_2 + Q_1} = xQ_2\bar{Q}_1$$

$$Q_1^* = D_1 = x$$


Mealy

$$Q_2^* = D_2 = \overline{x + Q_2 + \bar{Q}_1} = \bar{x} \bar{Q}_2 Q_1$$

状态表

 


【练习2】时序电路分析

 

激励方程: $D = A \oplus x \oplus y$

状态方程: $A^* = A \oplus x \oplus y$



Present state	Inputs		Next state
A	x	y	A^*
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

 


2

F S M


流水灯

  

 

```
1 module WaterLED( input logic clk, reset,  
2                   output logic [15:0] led );  
3     parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3, S4 = 4,  
4               S5 = 5, S6 = 6, S7 = 7, S8 = 8;  
5     logic [3:0] state;  
6  
7     always_ff @(posedge clk)  
8         if (!reset) state <= S0;  
9         else case (state)  
10             S0: state <= S1; S1: state <= S2; S2: state <= S3;  
11             S3: state <= S4; S4: state <= S5; S5: state <= S6;  
12             S6: state <= S7; S7: state <= S8; S8: state <= S0;  
13             default: state <= S0;  
14         endcase  
15  
16     always_comb  
17         case (state) // 从两边往中间逐个亮  
18             S0 : led = 16'b0000_0000_0000_0000;  
19             S1 : led = 16'b1000_0000_0000_0001;  
20             S2 : led = 16'b1100_0000_0000_0011;  
21             S3 : led = 16'b1110_0000_0000_0111;  
22             S4 : led = 16'b1111_0000_0000_1111;  
23             S5 : led = 16'b1111_1000_0001_1111;  
24             S6 : led = 16'b1111_1100_0011_1111;  
25             S7 : led = 16'b1111_1110_0111_1111;  
26             S8 : led = 16'b1111_1111_1111_1111;  
27             default: led = 16'b0000_0000_0000_0000; //全灭  
28         endcase  
29 endmodule
```


流水灯 原理图

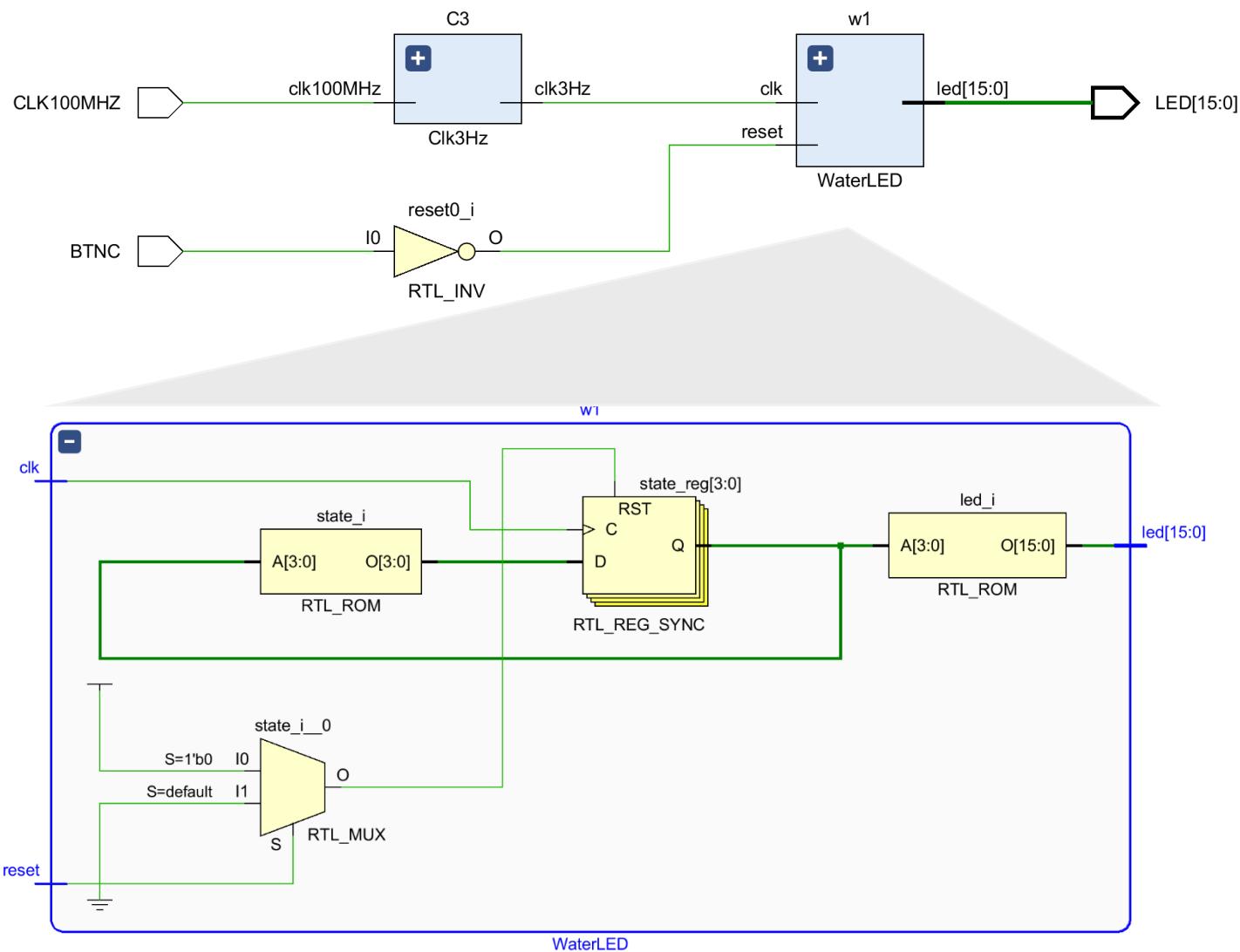


```

1  module WaterLED( input logic clk, reset,
2                    output logic [15:0] led );
3      parameter S0 = 0, S1 = 1, S2 = 2, S3 = 3, S4 = 4,
4                  S5 = 5, S6 = 6, S7 = 7, S8 = 8;
5      logic [3:0] state;
6
7      always_ff @(posedge clk)
8          if (!reset) state <= S0;
9          else case (state)
10              S0: state <= S1; S1: state <= S2; S2: state <= S3;
11              S3: state <= S4; S4: state <= S5; S5: state <= S6;
12              S6: state <= S7; S7: state <= S8; S8: state <= S0;
13              default: state <= S0;
14          endcase
15
16      always_comb
17          case (state) // 从两边往中间逐个亮
18              S0 : led = 16'b0000_0000_0000_0000;
19              S1 : led = 16'b1000_0000_0000_0001;
20              S2 : led = 16'b1100_0000_0000_0011;
21              S3 : led = 16'b1110_0000_0000_0111;
22              S4 : led = 16'b1111_0000_0000_1111;
23              S5 : led = 16'b1111_1000_0001_1111;
24              S6 : led = 16'b1111_1100_0011_1111;
25              S7 : led = 16'b1111_1110_0111_1111;
26              S8 : led = 16'b1111_1111_1111_1111;
27              default: led = 16'b0000_0000_0000_0000; //全灭
28          endcase
29  endmodule

```


有限状态机 Finite State Machine

 - 电路设计**经典方法**，尤其适于设计控制模块，易于FPGA实现。
- 用于：对有限内部状态相互转换的系统进行建模。
- 常为同步时序，在时钟信号的触发下完成各状态之间的转换，并产生相应的输出。
- 由组合逻辑(**状态译码、产生输出信号**) + 时序逻辑(**存储状态**)构成。
- 状态机表示方法：**状态图**、状态表、流程图。三者等价。




FSM 分类

经典状态机

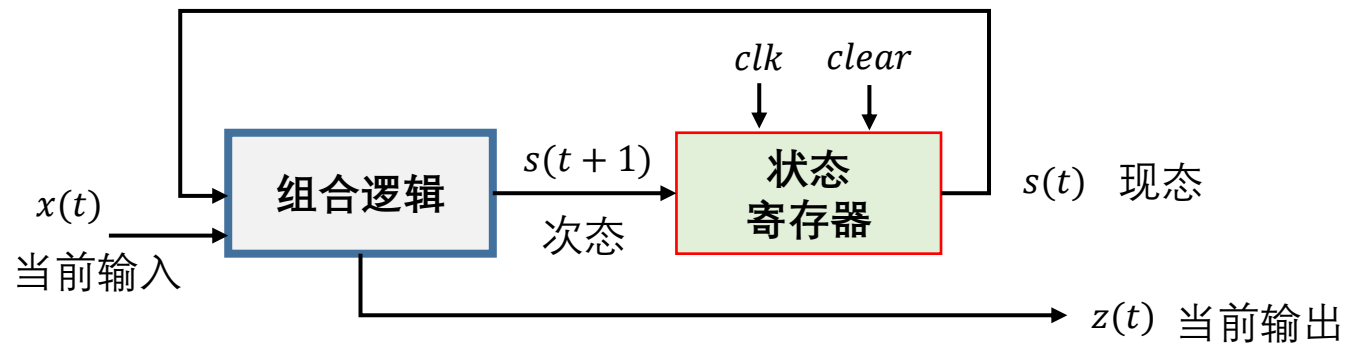


摩尔状态机

 


同一系统，
既可以用摩尔模型描述
也可以用米里模型描述

米里状态机

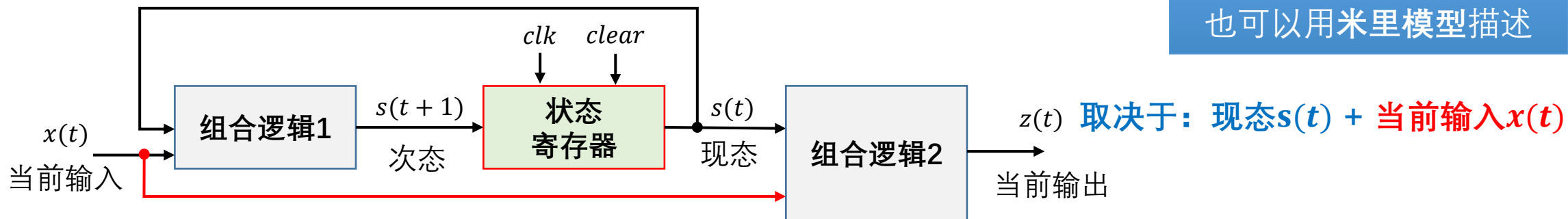

复杂系统：混合编程

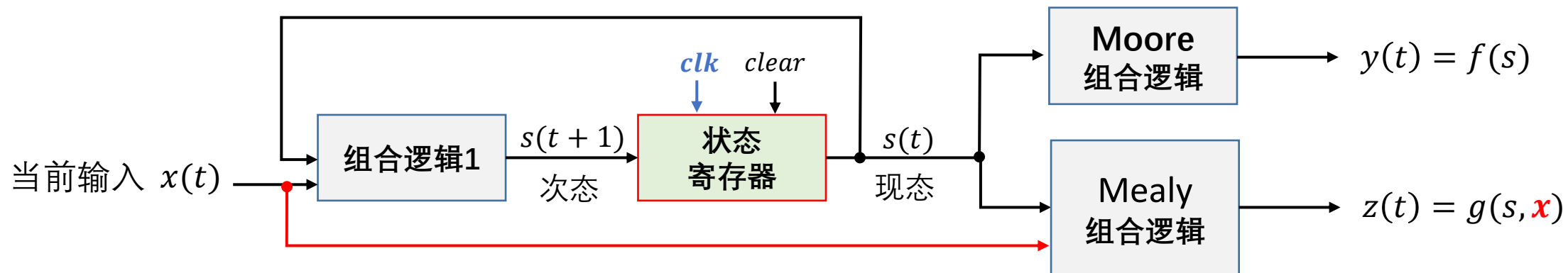

// Moore


```
assign y = (state == s0) || (state == s1);
```

// Mealy


```
assign z = (state == s0) & x;
```

1101序列检测器：状态机

摩尔状态机

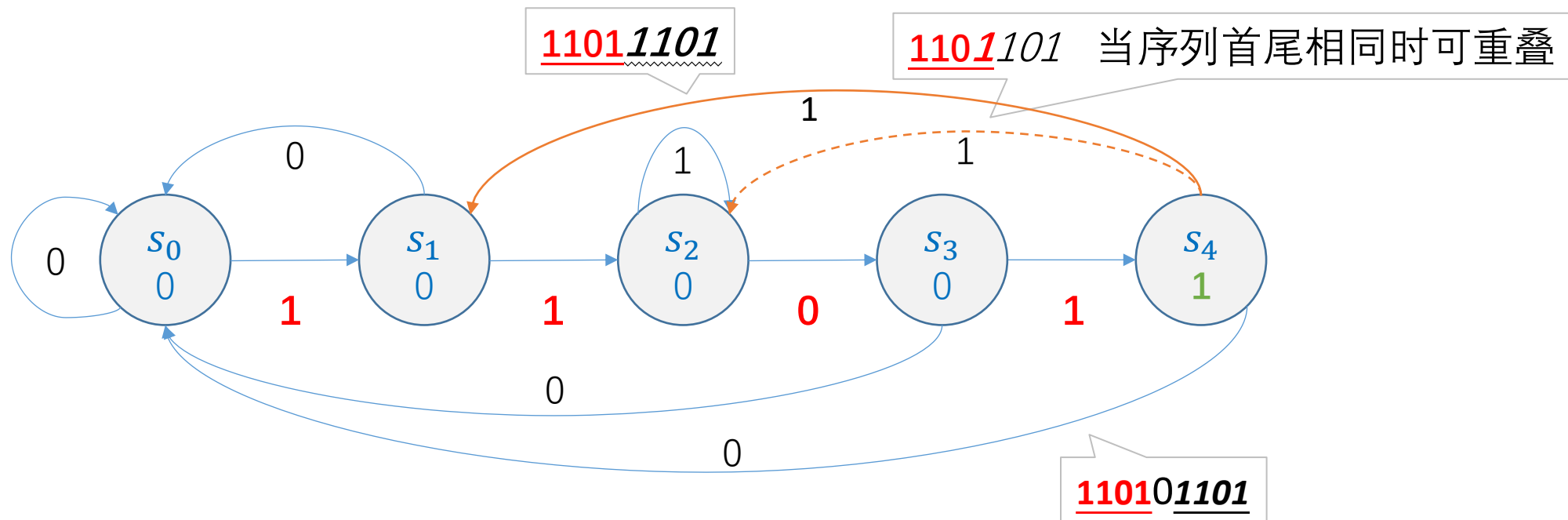

米里状态机

 

FSM设计要点



- 状态机有3部分：①当前状态 PS、②下一状态 NS、③输出逻辑 OL。
- Verilog有4种描述方式：
 - 三段式：①、②、③各用一个 always / assign 描述；
 - 两段式：① + ②、③ 或 ②、① + ③ 各用一个always；
 - 一段式：① + ② + ③ 只用一个always。
- 多余状态要明确定义，或者用case语句中的default。
- 初始状态：电路复位后所处的状态。

实用的状态机都应有**复位信号**。
- 异步复位比同步复位占用更少的额外资源。

1101序列检测器 Moore

FSM

三段式描述

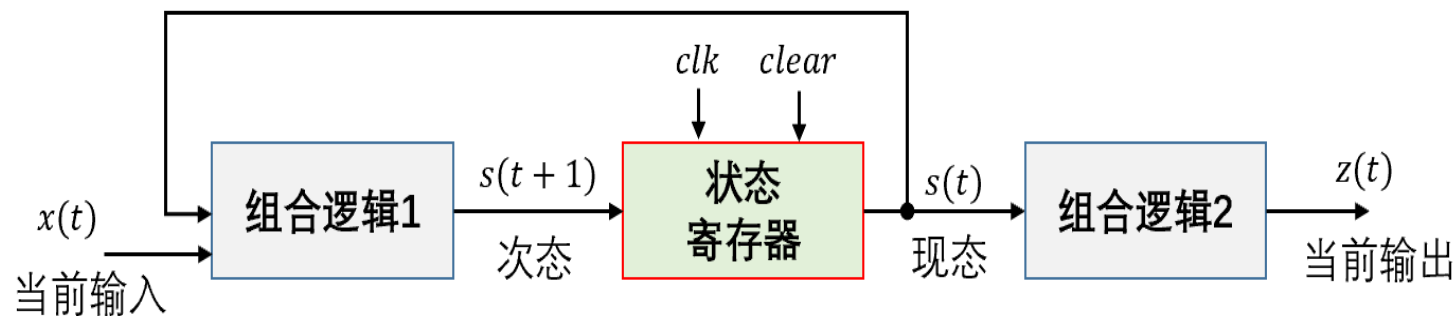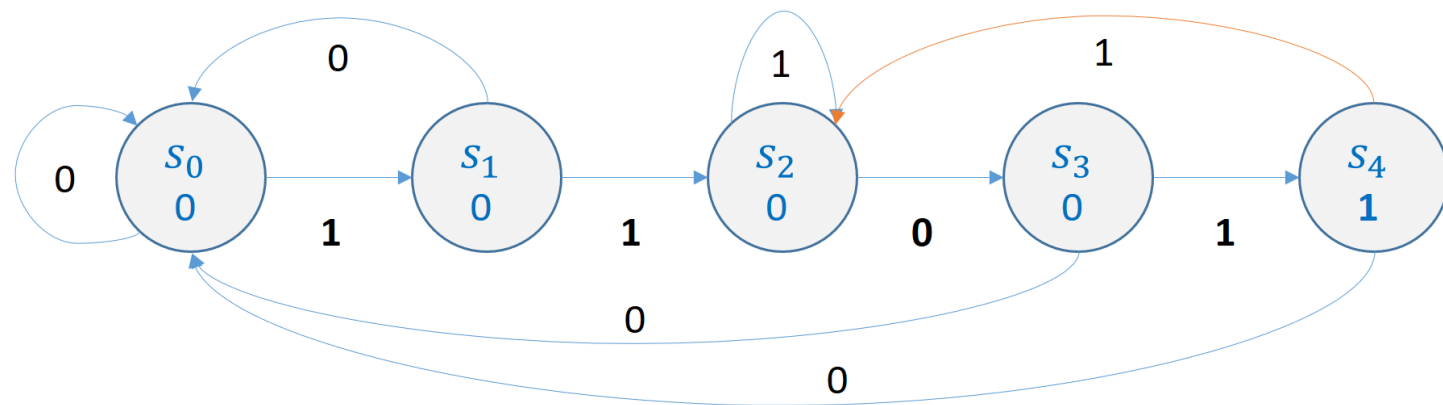

```
2 module Detect1101_Moore(input logic clk, clr, Din,  
3                          output logic Dout );  
4     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
5               S3=3'b011, S4=3'b100; // 状态  
6     logic [2:0] present_state, next_state;
```

```
8     always_comb // 次态 组合逻辑1  
9         case (present_state)  
10             S0: if(Din==1) next_state = S1; ①  
11                 else next_state = S0;  
12             S1: if(Din==1) next_state = S2;  
13                 else next_state = S0;  
14             S2: if(Din==0) next_state = S3;  
15                 else next_state = S2;  
16             S3: if(Din==1) next_state = S4;  
17                 else next_state = S0;  
18             S4: if(Din==0) next_state = S0;  
19                 else next_state = S2;  
20             default: next_state = S0;  
21         endcase
```

```
22     always_ff @(posedge clk, posedge clr) 状态寄存器  
23         if(clr==1) present_state <= S0; ②  
24         else present_state <= next_state;
```



```
26     always_comb // 输出逻辑 组合逻辑2  
27         if(present_state==S4) Dout = 1; ③  
28         else Dout = 0;
```

```
30 endmodule
```

1101序列检测器 Mealy

FSM

三段式描述

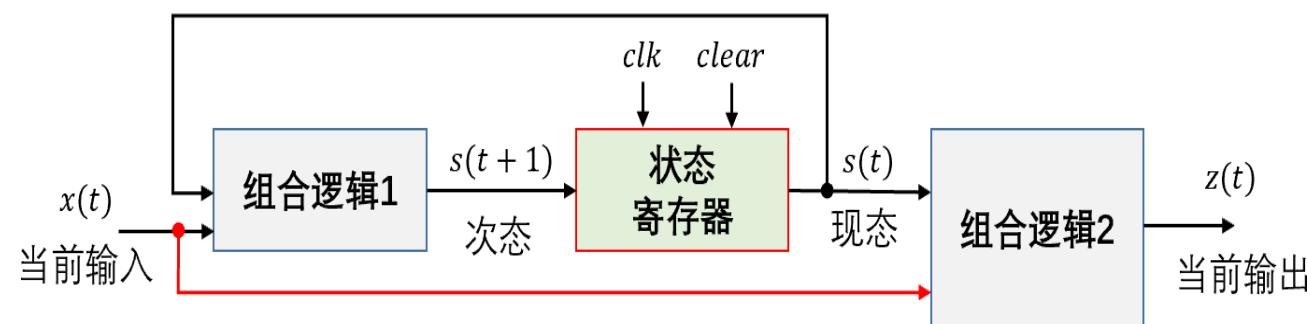 

s_3 的输出 $Dout$ 需要寄存，故用时序电路！

```
module Detect1101_Mealy(input logic clk, clr,
                        input logic Din,
                        output logic Dout ); // reg!!
    parameter S0=2'b00, S1=2'b01, S2=2'b10, S3=2'b11;
    logic [1:0] present_state, next_state; //reg
```

```
    always_comb // 次状态
    case (present_state)
        S0: if(Din==1) next_state = S1;
            else next_state = S0;
        S1: if(Din==1) next_state = S2;
            else next_state = S0;
        S2: if(Din==0) next_state = S3;
            else next_state = S2;
        S3: if(Din==1) next_state = S1;
            else next_state = S0;
        default: next_state = S0;
    endcase
```

组合逻辑1

①

```
    always_ff @(posedge clk, posedge clr)
        if(clr==1) present_state <= S0;
        else present_state <= next_state;
```

状态寄存器

②

```
    always_ff @(posedge clk) // 输出逻辑 组合逻辑2
        if((present_state==S3) && (Din==1)) Dout <= 1;
        else Dout <= 0;
```

组合逻辑2

③


```
endmodule
```


1101序列检测器：板级验证

```

1 module DetectSequence_Top(
2     input logic CLK100MHZ,
3     input logic BTNC, // clr
4     input logic BTNL, // 0
5     input logic BTNR, // 1
6     output logic [0:0] LED );
7
8     logic clr, clk190Hz, clkp, btn01;
9
10    assign clr = BTNC;
11    assign btn01 = BTNL | BTNR;
12
13    clkdiv U1(.mclk(CLK100MHZ), .clr(clr),
14              .clk190Hz(clk190Hz));
15
16    clock_pulse U2(.inp(btn01), .cclk(clk190Hz),
17                  .clr(clr), .outp(clkp));
18
19    Detect1101_Mealy D1(.clk(clkp),
20                      .clr(clr),
21                      .Din(BTNR),
22                      .Dout(LED[0]));
23 endmodule

```

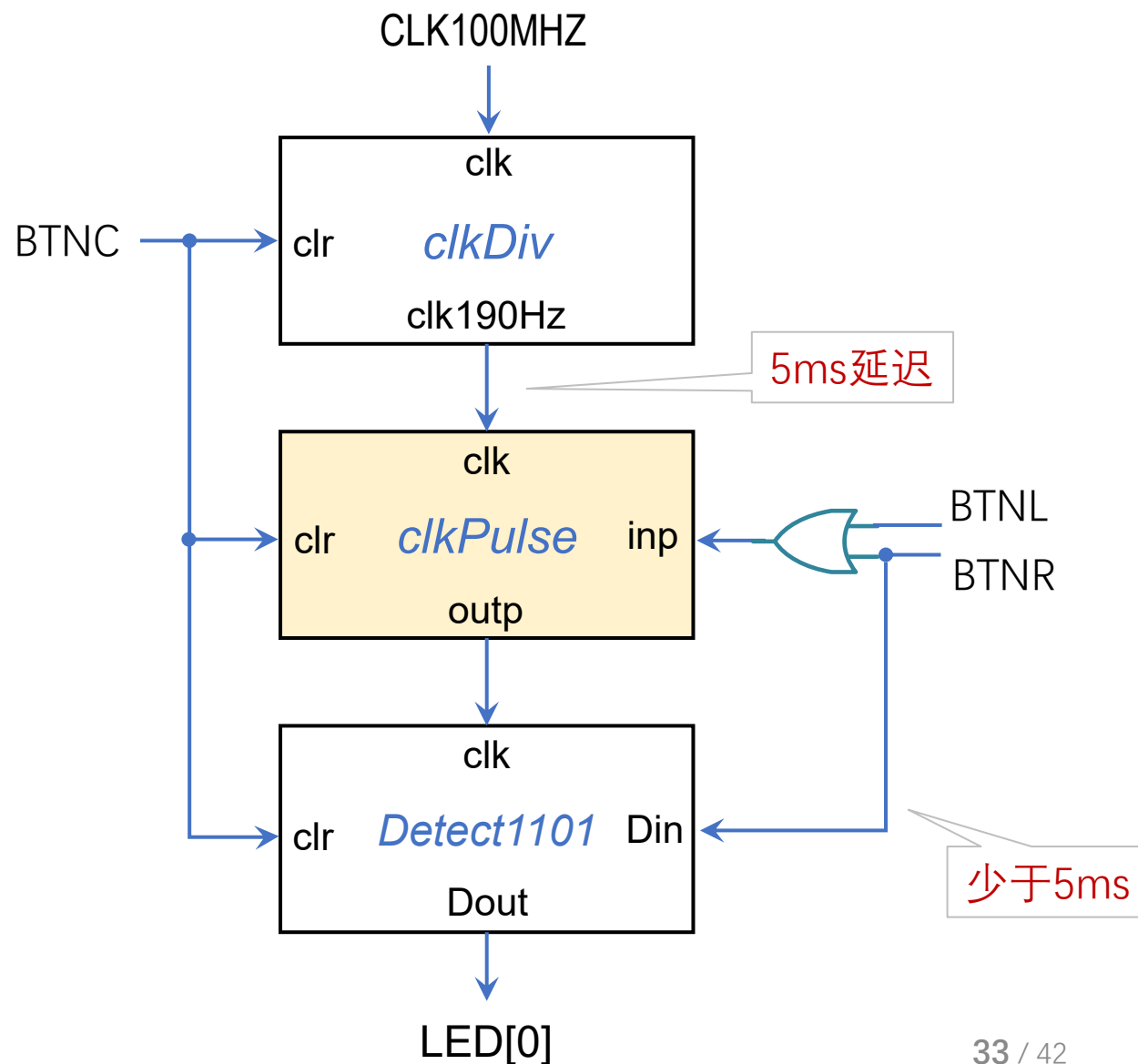

1101序列检测器 Moore-2

```
2 module Detect1101_Moore(input logic clk, clr, Din,  
3                          output logic Dout );  
4     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
5               S3=3'b011, S4=3'b100; // 状态  
6     logic [2:0] present_state, next_state;
```

组合逻辑1

```
8     always_comb // 次态  
9         case (present_state)  
10             S0: if(Din==1) next_state = S1;  
11                 else next_state = S0;  
12             S1: if(Din==1) next_state = S2;  
13                 else next_state = S0;  
14             S2: if(Din==0) next_state = S3;  
15                 else next_state = S0;  
16             S3: if(Din==1) next_state = S4;  
17                 else next_state = S0;  
18             S4: if(Din==0) next_state = S0;  
19                 else next_state = S2;  
20             default: next_state = S0;  
21         endcase
```

三段式

状态寄存器

```
22     always_ff @(posedge clk, posedge clr)  
23         if(clr==1) present_state <= S0;  
24         else present_state <= next_state;
```

组合逻辑2

```
25     always_comb // 输出逻辑  
26         if(present_state==S4) Dout = 1;  
27         else Dout = 0;
```

```
28 endmodule
```

```
2 module D1101_Moore2_1(input logic clk, clr, Din,  
3                        output logic Dout );  
4     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
5               S3=3'b011, S4=3'b100;  
6     logic [2:0] present_state; //next_state;
```

合并① ②


```
7     always_ff @(posedge clk, posedge clr)  
8         if(clr==1) present_state <= S0;  
9         else case (present_state)  
10             S0: if(Din==1) present_state <= S1;  
11                 else present_state <= S0;  
12             S1: if(Din==1) present_state <= S2;  
13                 else present_state <= S0;  
14             S2: if(Din==0) present_state <= S3;  
15                 else present_state <= S2;  
16             S3: if(Din==1) present_state <= S4;  
17                 else present_state <= S0;  
18             S4: if(Din==0) present_state <= S0;  
19                 else present_state <= S2;  
20             default: present_state <= S0;  
21         endcase
```

组合逻辑2

```
22     always_comb // 输出逻辑  
23         if(present_state==S4) Dout = 1;  
24         else Dout = 0;
```

```
25 endmodule
```

两段式描述

 

1101序列检测器 Moore-3

```
2 module Detect1101_Moore(input logic clk, clr, Din,  
3                          output logic Dout );  
4     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
5               S3=3'b011, S4=3'b100; // 状态  
6     logic [2:0] present_state, next_state;
```

always_comb // 次态 **组合逻辑1**

case (present_state)

S0: if(Din==1) next_state = S1;

else next_state = S0;

S1: if(Din==1) next_state = S2;

else next_state = S0;

S2: if(Din==0) next_state = S3;

else next_state = S2;

S3: if(Din==1) next_state = S4;

else next_state = S0;

S4: if(Din==0) next_state = S0;

else next_state = S2;

default: next_state = S0;

endcase

always_ff @(posedge clk, posedge clr)

if(clr==1) present_state <= S0;

else present_state <= next_state;

always_comb // 输出逻辑

if(present_state==S4) Dout = 1;

else Dout = 0;

endmodule

```
2 module D1101_Moore2_2(input logic clk, clr, Din,  
3                          output logic Dout );  
4     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
5               S3=3'b011, S4=3'b100; // 状态  
6     logic [2:0] present_state, next_state;
```

always_ff @(posedge clk, posedge clr)

if(clr==1) present_state <= S0;

else present_state <= next_state;

always_comb

case (present_state)

S0: if(Din==1) begin next_state = S1; Dout = 0; end

else begin next_state = S0; Dout = 0; end

S1: if(Din==1) begin next_state = S2; Dout = 0; end

else begin next_state = S0; Dout = 0; end

S2: if(Din==0) begin next_state = S3; Dout = 0; end

else begin next_state = S2; Dout = 0; end

S3: if(Din==1) begin next_state = S4; Dout = 0; end

else begin next_state = S0; Dout = 0; end


S4: if(Din==0) begin next_state = S0; Dout = 1; end

else begin next_state = S2; Dout = 1; end

default: begin next_state = S0; Dout = 0; end

endcase

endmodule

 

两段式描述

合并① ③

1101序列检测器 Moore-4

```
2 module Detect1101_Moore(input logic clk, clr, Din,  
3                          output logic Dout );  
4     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
5               S3=3'b011, S4=3'b100; // 状态  
6     logic [2:0] present_state, next_state;
```

always_comb // 次态 组合逻辑1

case (present_state)

S0: if(Din==1) next_state = S1;

else next_state = S0;

S1: if(Din==1) next_state = S2;

else next_state = S0;

S2: if(Din==0) next_state = S3;

else next_state = S2;

S3: if(Din==1) next_state = S4;

else next_state = S0;

S4: if(Din==0) next_state = S0;

else next_state = S2;

default: next_state = S0;

endcase

always_ff @(posedge clk, posedge clr)

if(clr==1) present_state <= S0;

else present_state <= next_state;

always_comb // 输出逻辑

if(present_state==S4) Dout = 1;

else Dout = 0;

endmodule

```
2 module D1101_Moore3(input logic clk, clr, Din,  
3                     output logic Dout );  
4  
5     parameter S0=3'b000, S1=3'b001, S2=3'b010,  
6               S3=3'b011, S4=3'b100; // 状态  
7  
8     logic [2:0] present_state; // next_state;
```

always_ff @(posedge clk, posedge clr)

if(clr==1) begin present_state <= S0; Dout <= 0; end

else case (present_state)

S0: if(Din==1) begin present_state <= S1; Dout <= 0; end

else begin present_state <= S0; Dout <= 0; end

S1: if(Din==1) begin present_state <= S2; Dout <= 0; end

else begin present_state <= S0; Dout <= 0; end

S2: if(Din==0) begin present_state <= S3; Dout <= 0; end

else begin present_state <= S2; Dout <= 0; end

S3: if(Din==1) begin present_state <= S4; Dout <= 1; end

else begin present_state <= S0; Dout <= 0; end


S4: if(Din==0) begin present_state <= S0; Dout <= 0; end

else begin present_state <= S2; Dout <= 0; end

default: begin present_state <= S0; Dout <= 0; end

endcase

endmodule

 

合并①②③



一段式

3


去抖电路

机械抖动

 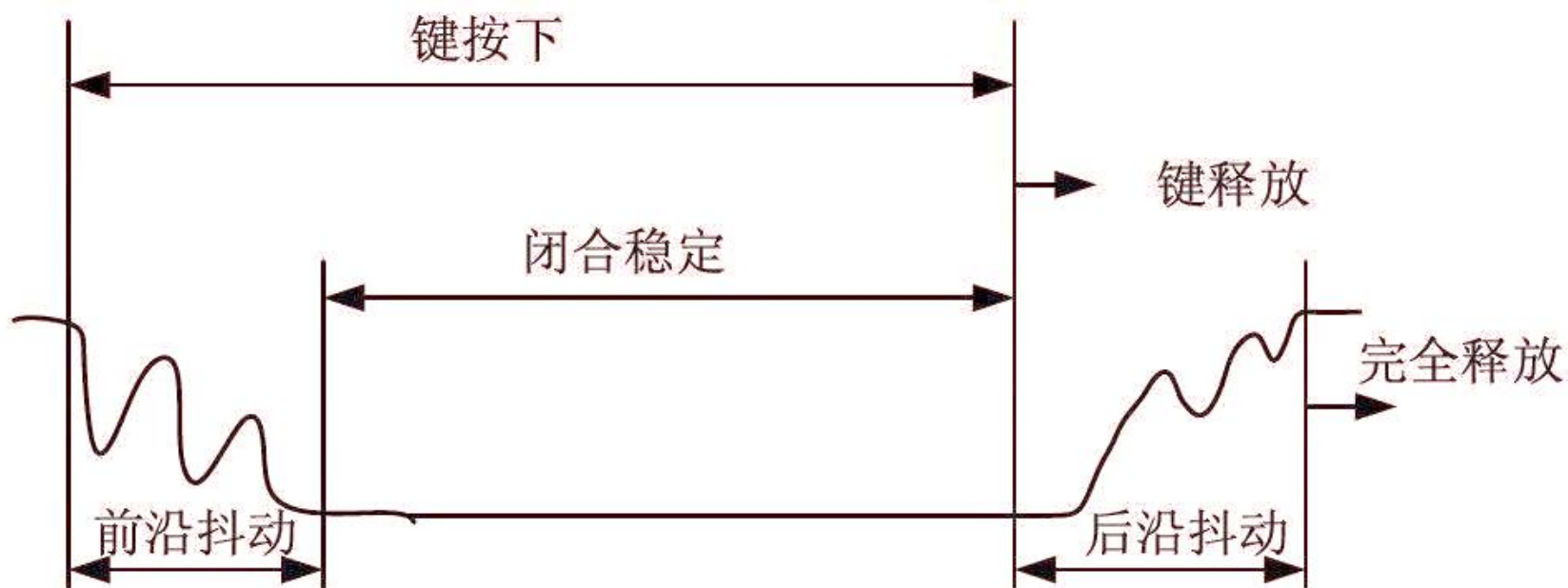
- 任何按钮，按动之后，在稳定下来之前都会有几毫秒的抖动。
- 可能将抖动的错误值锁存到寄存器中！



去抖电路

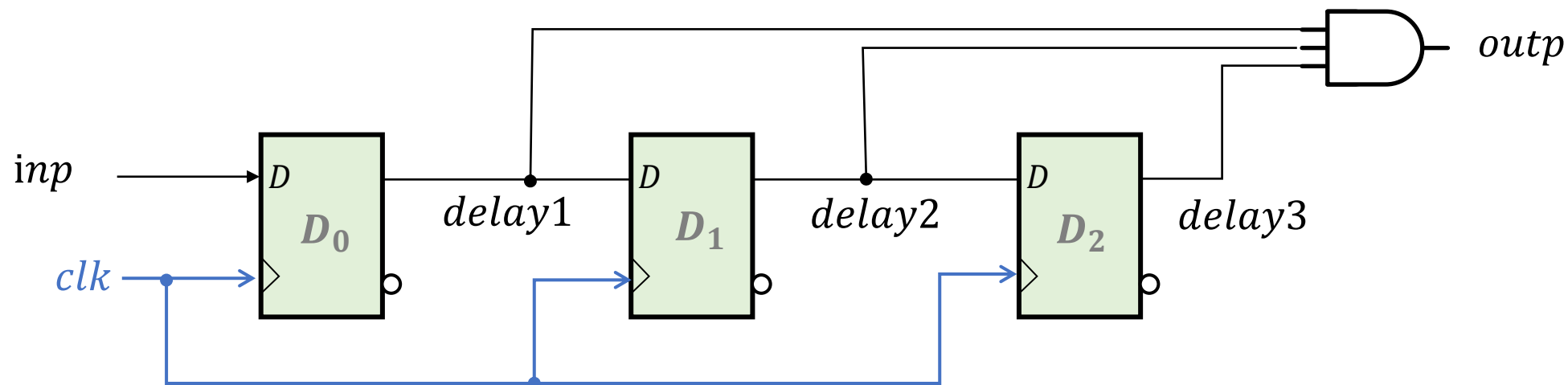

【注】时钟要足够慢。保证抖动在3个时钟周期内！如 clk_190Hz

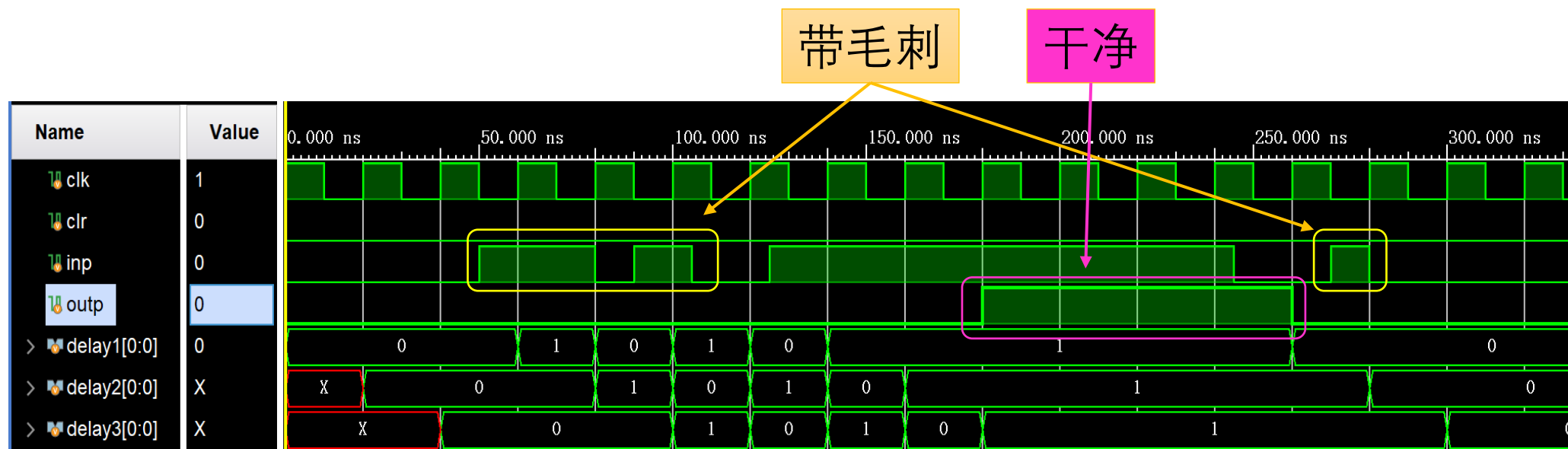



Debounce

去抖代码

```

2 module Debounce #(parameter N = 1)
3   ( input logic clk, clr,
4     input logic [N-1:0] inp,
5     output logic [N-1:0] outp );
6
7   logic [N-1:0] delay1, delay2, delay3;
8
9   always_ff @(posedge clk, posedge clr)
10  begin
11    if(clr) begin
12      delay1 <= 0;
13      delay2 <= 0;
14      delay3 <= 0;
15    end
16    else begin
17      delay1 <= inp;
18      delay2 <= delay1;
19      delay3 <= delay2;
20    end
21
22    assign outp = delay1 & delay2 & delay3;
23  end
24 endmodule

```

 
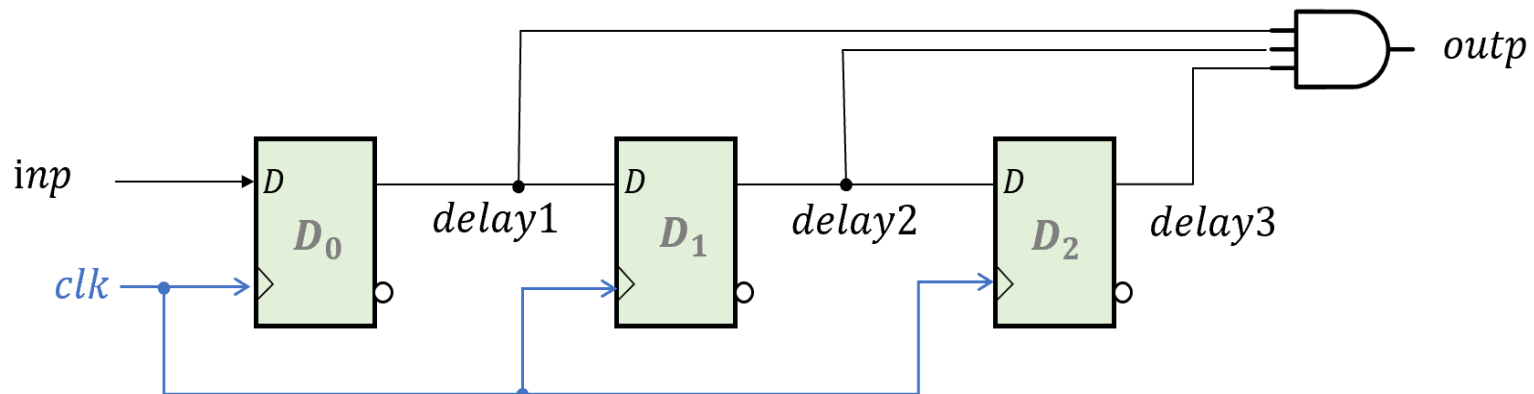


```

1 timescale 1ns / 1ps
2 module Debounce_Sim( );
3   logic clk, clr, inp, outp;
4   // 实例化
5   Debounce D1(clk, clr, inp, outp);
6
7   always //时钟
8   begin
9     clk = 1; #10; clk = 0; #10;
10  end
11
12  initial //输入值
13  begin
14    clr = 0; inp = 0;
15    #50; inp = 1; #30; inp = 0;
16    #10; inp = 1; #15; inp = 0;
17    #20; inp = 1; #120; inp = 0;
18    #25; inp = 1; #10; inp = 0;
19  end
20 endmodule

```


时钟脉冲：按一次键，产生一个单脉冲

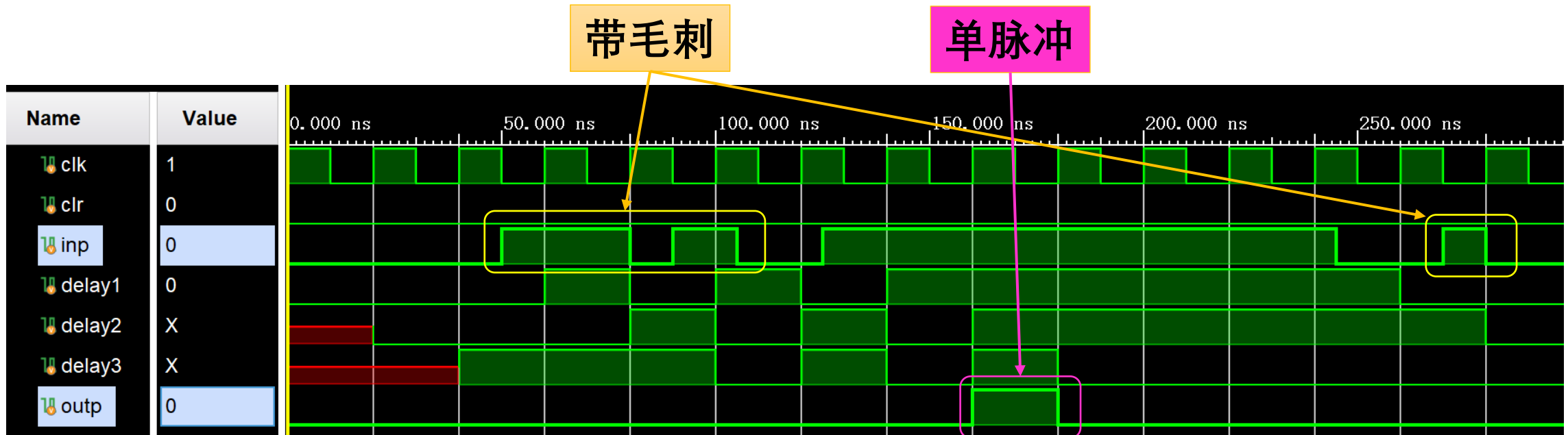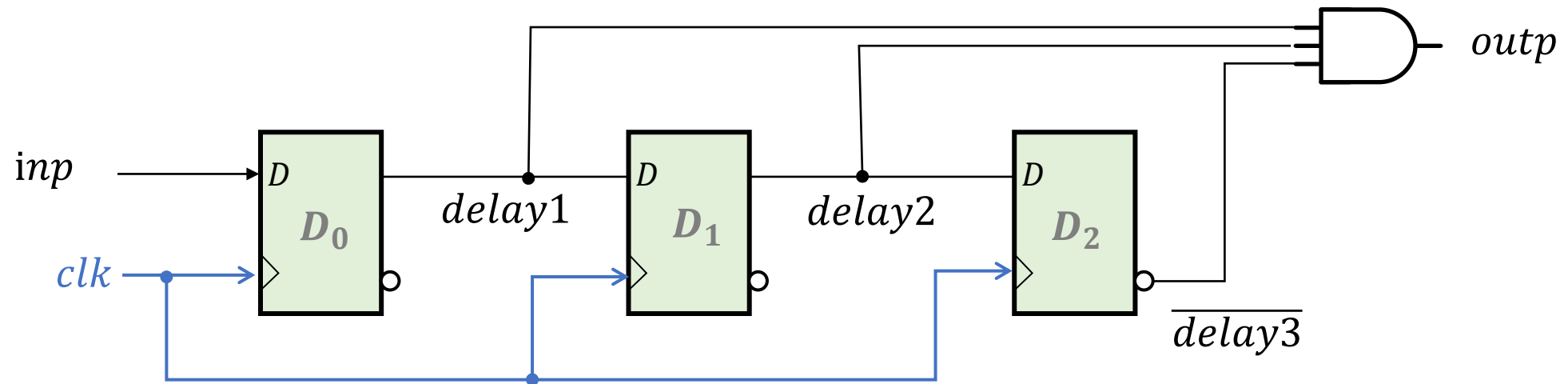


单脉冲代码

```

1  module ClockPulse(input logic clk, clr,
2      input logic inp,
3      output logic outp );
4
5      logic delay1, delay2, delay3;
6
7      always_ff @(posedge clk, posedge clr)
8      begin
9          if(clr) begin
10             delay1 <= 0;
11             delay2 <= 0;
12             delay3 <= 0;          end
13          else begin
14             delay1 <= inp;
15             delay2 <= delay1;
16             delay3 <= ~delay2; end
17      end
18
19      assign outp = delay1 & delay2 & delay3;
20  endmodule

```

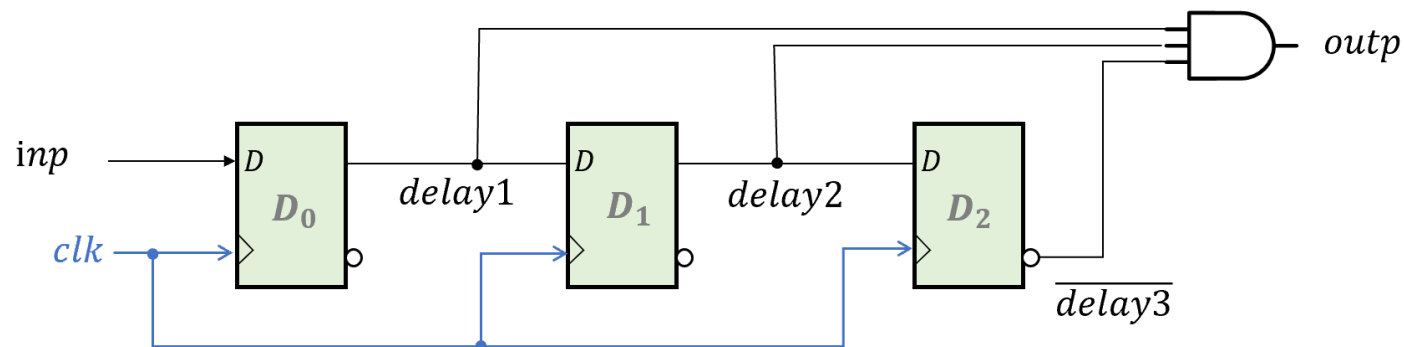

```

1  `timescale 1ns / 1ps
2  module ClockPulse_Sim();
3      logic clk, clr, inp, outp;
4
5      ClockPulse C1(clk, clr, inp, outp);
6
7      always //时钟
8      begin
9          clk = 1; #10; clk = 0; #10;
10     end
11
12     initial //输入值
13     begin
14         clr = 0; inp = 0;
15         #50; inp = 1; #30; inp = 0;
16         #10; inp = 1; #15; inp = 0;
17         #20; inp = 1; #120; inp = 0;
18         #25; inp = 1; #10; inp = 0;
19     end
20 endmodule

```