 


# 实验2：七段LED数码管



[xgsun@fudan.edu.cn](mailto:xgsun@fudan.edu.cn)

孙晓光

2024-9-8




1

NEXYS 4


# 简介

通过USB供电、编程以及串口监视， 只需1根USB线

 
 
# Nexys4 DDR 特点



- 10/100 Ethernet PHY
- 128Mib DDR2
- SD卡插槽（可用来存储FPGA程序）
- Micro USB接口（UART和编程口共用）
- USB HID主机接口（鼠标、键盘）
- Digilent USB-JTAG port for FPGA programming & communication
- 4个Pmod接口、 Pmod for XADC signals
- USB HID Host for mice, keyboards and memory sticks
- **PWM (Pulse Width Modulation)音频输出**
- PDM（脉冲密度调制）数字麦克风
- **基本IO： 16路拨码开关、16路LED、8路七段LED数码管**  
**2个RGB 三色 LED、5个按钮**



- **12位VGA接口**
- 温度传感器
- 串行Flash
- 3轴加速度计



# Pmod接口\*

  

96x64,16位色彩分辨率RGB OLED屏



带16个按键的键盘



带有并行接口的字符型LCD<sup>5</sup>

# XC7A100T

Artix-7, Spartan-7, Kintex-7, Virtex-7

**Artix-7**是**7系列**中低成本系列芯片，  
面向成本敏感型应用FPGA，具有目前最低的成本和功耗优势，  
特别适用于消费类电子以及手持和便携设备。




Xilinx(赛灵思)公司

**XC7A100T**是Artix-7系列中资源比较丰富的一款芯片


- 15,850 logic slices, each with four **6-input LUTs** and **8 flip-flops**
- 4,860 Kbits快速随机存储器RAM
- Six clock management tiles, each with phase-locked loop (PLL)
- 内部时钟速度超过450 MHz
- 240 DSP(数字信号处理) slices(切片)
- 片上模数转换器 (XADC)
 
# FPGA 现场可编程门阵列

- FPGA：可由用户现场进行编程的大规模电路。
- FPGA是80年代中期发展起来的一种可编程的。
- 特点：
  - 保密性强
  - 体积小
  - 可靠性高




# 通用FPGA结构图

 

LE: 逻辑单元


LUT: Look-up Table

 

<b>a</b>	<b>b</b>	<b>c</b>	<b>y</b>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1




# Altera's Cyclone IV LE

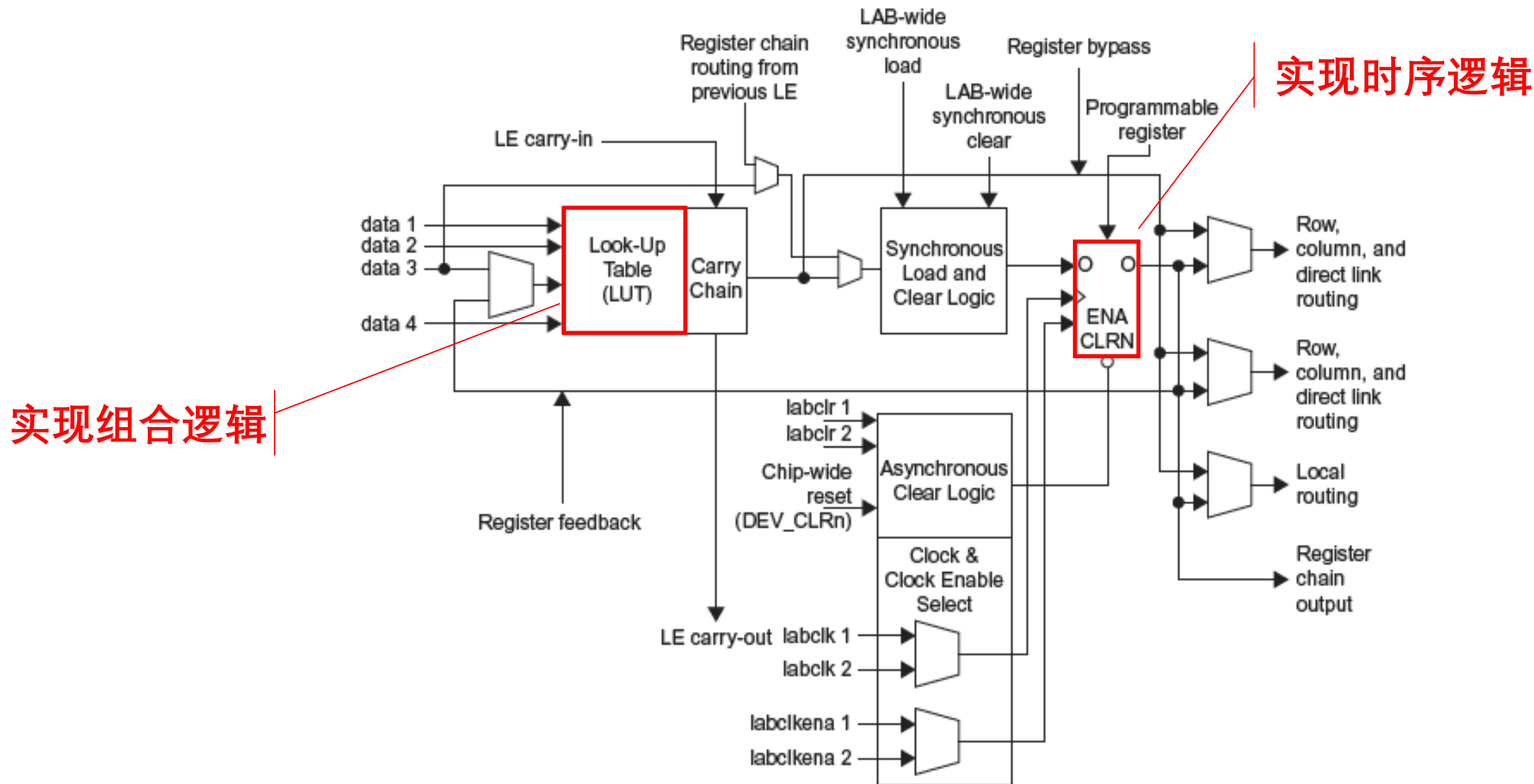


2

# 基本 IO

# XC7A100T

 


# 基本IO

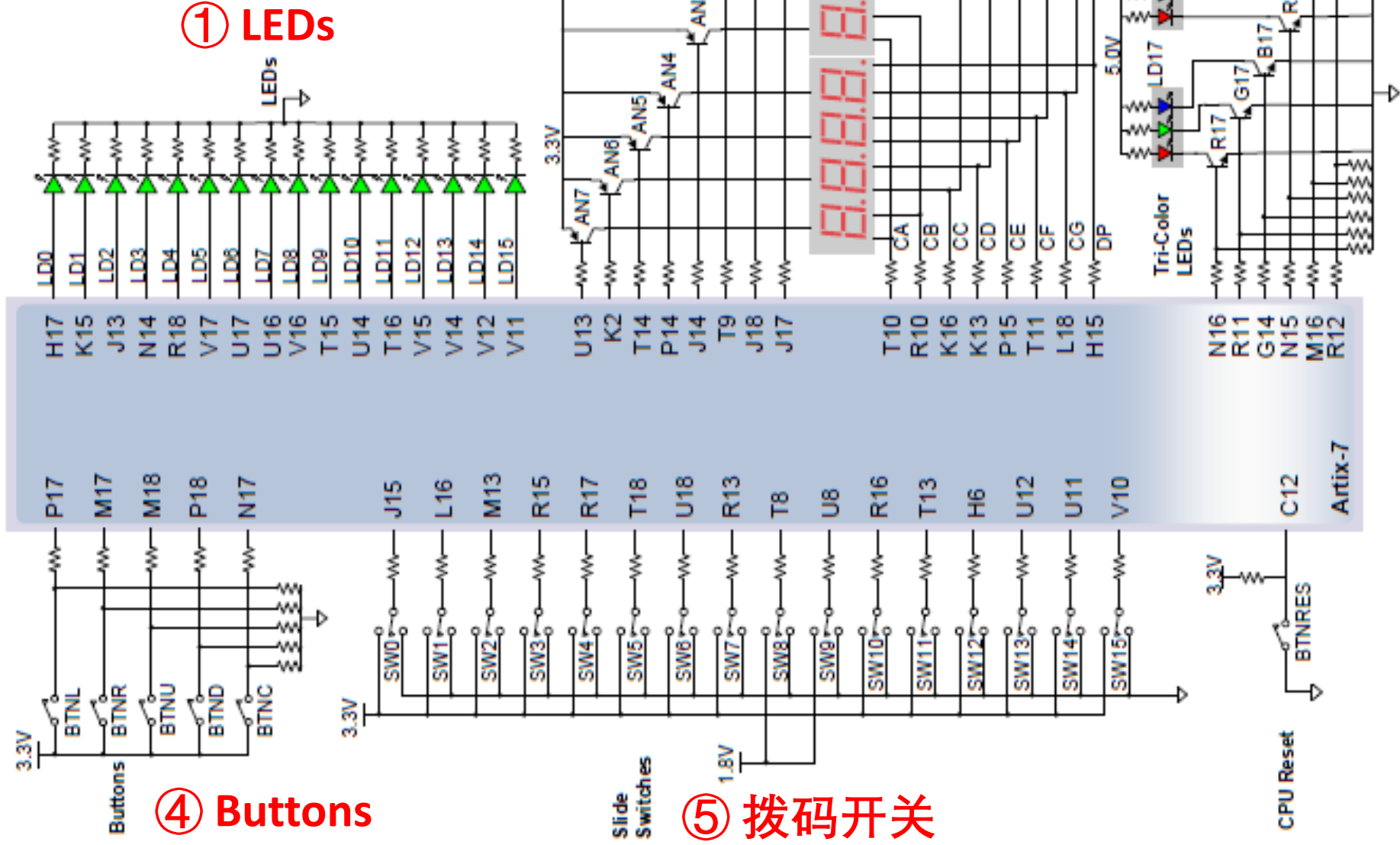



# ① LEDs + Switches

 

当一个正向电流通过发光二极管(LED)时，LED就会发光。

FPGA的I/O引脚有**2种**方式点亮LED:


① LED右端 $V_1$ 接地

- 点亮LED， $V_2$ 端为高电平(**1**)
- 熄灭LED， $V_2$ 端为低电平(**0**)

② LED左端 $V_2$ 接恒定电压

- 点亮LED， $V_1$ 端为低电平(**0**)
- 熄灭LED， $V_1$ 端为高电平(**1**)


Artix-7

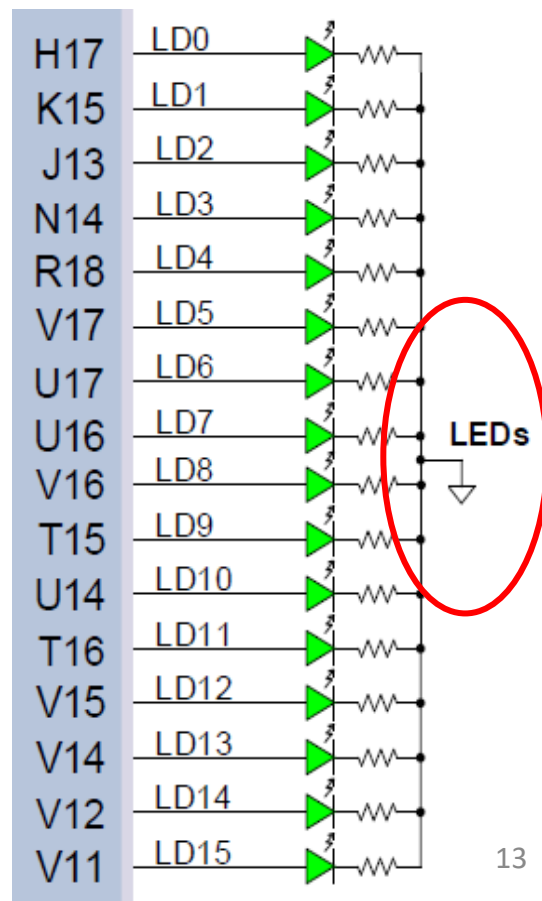
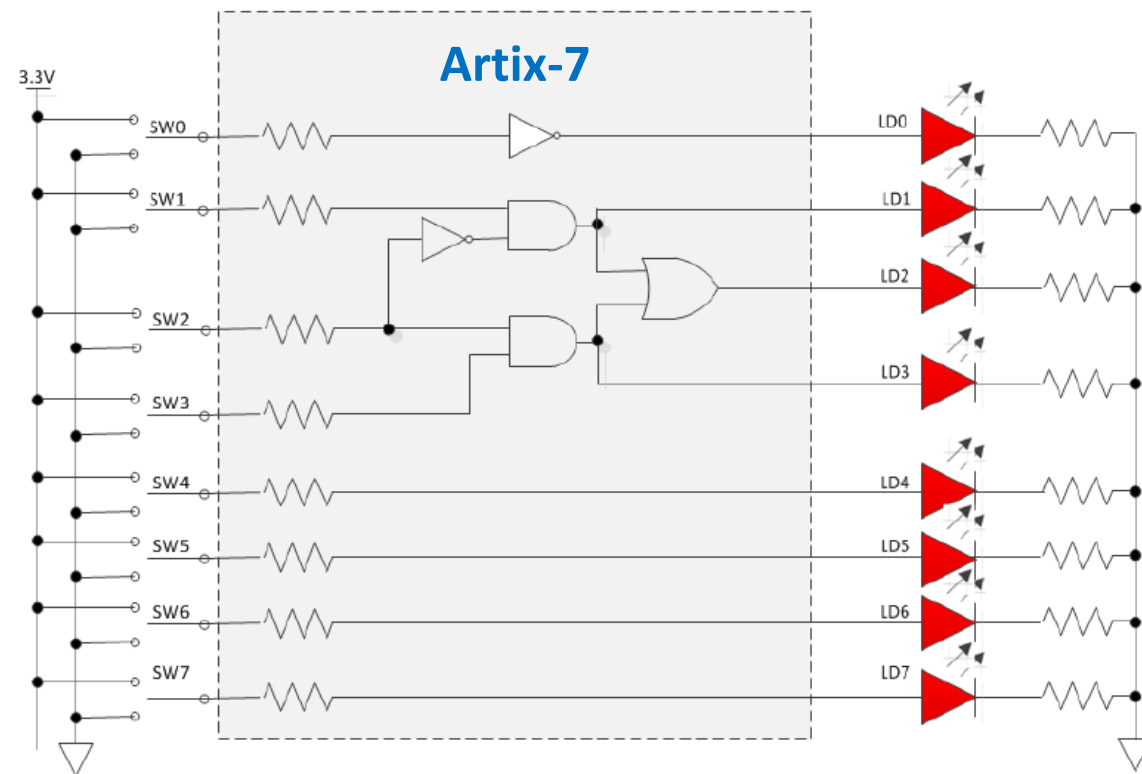
## 例：点亮LED

Leds.sv

```
1 module Leds(  
2     input logic [3:0] SW,  
3     output logic [3:0] LED;  
4  
5     assign LED = SW;  
6 endmodule
```




Nexys4DDR\_Master.xdc

```
1 ##Switches  
2 set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { SW[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]  
3 set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { SW[1] }]; #IO_L3N_T0_DQS_EMCCCLK_14 Sch=sw[1]  
4 set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { SW[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]  
5 set_property -dict { PACKAGE_PIN R15 IOSTANDARD LVCMOS33 } [get_ports { SW[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]  
6  
7 ## LEDs  
8 set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { LED[0] }]; #IO_L18P_T2_A24_15 Sch=led[0]  
9 set_property -dict { PACKAGE_PIN K15 IOSTANDARD LVCMOS33 } [get_ports { LED[1] }]; #IO_L24P_T3_RS1_15 Sch=led[1]  
10 set_property -dict { PACKAGE_PIN J13 IOSTANDARD LVCMOS33 } [get_ports { LED[2] }]; #IO_L17N_T2_A25_15 Sch=led[2]  
11 set_property -dict { PACKAGE_PIN N14 IOSTANDARD LVCMOS33 } [get_ports { LED[3] }]; #IO_L8P_T1_D11_14 Sch=led[3]
```
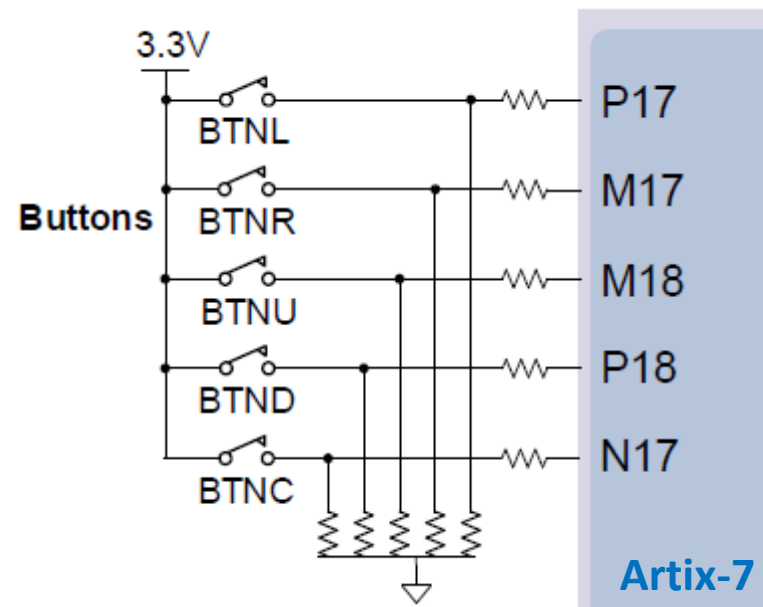
## ② Buttons 示例代码

Button.sv

```
1 module Button(  
2     input logic BTNC,  
3     output logic [0:0] LED);  
4  
5     assign LED[0] = BTNC;  
6 endmodule
```




Nexys4DDR\_Master.xdc

```
1 ## LEDs  
2 set_property -dict { PACKAGE_PIN H17 IOSTANDARD LVCMOS33 } [get_ports { LED[0] }]; #IO_L18P_T2_A24_15 Sch=led[0]  
3  
4 ##Buttons  
5 set_property -dict { PACKAGE_PIN N17 IOSTANDARD LVCMOS33 } [get_ports { BTNC }]; #IO_L9P_T1_DQS_14 Sch=btnc  
6 #set_property -dict { PACKAGE_PIN M18 IOSTANDARD LVCMOS33 } [get_ports { BTNU }]; #IO_L4N_T0_D05_14 Sch=btnu  
7 #set_property -dict { PACKAGE_PIN P17 IOSTANDARD LVCMOS33 } [get_ports { BTNL }]; #IO_L12P_T1_MRCC_14 Sch=btnl  
8 #set_property -dict { PACKAGE_PIN M17 IOSTANDARD LVCMOS33 } [get_ports { BTNR }]; #IO_L10N_T1_D15_14 Sch=btnr  
9 #set_property -dict { PACKAGE_PIN P18 IOSTANDARD LVCMOS33 } [get_ports { BTND }]; #IO_L9N_T1_DQS_D13_14 Sch=btnd  
10
```

## ③ Tri-Color LEDs 代码

```
ColorLED.sv
C:/Users/Sam/Documents/Vivado2015/ColorLED
1 module colorLED(
2   input logic [2:0] SW,
3   output logic LED16_B,
4   output logic LED16_G,
5   output logic LED16_R)
6
7   assign LED16_B = SW[0];
8   assign LED16_G = SW[1];
9   assign LED16_R = SW[2];
10 endmodule
```

三极管基极  
高电压时导通

 

```
Nexys4DDR_Master.xdc
C:/Users/Sam/Documents/Vivado2015/ColorLED/ColorLED.srcs/constrs_1/imports/01 XUP Nexys4 DDR Board/Nexys4DDR_Master.xdc
1 ##Switches
2 set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { SW[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]
3 set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { SW[1] }]; #IO_L3N_T0_DQS_EMCCCLK_14 Sch=sw[1]
4 set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { SW[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
5
6 ## LEDs
7 set_property -dict { PACKAGE_PIN R12 IOSTANDARD LVCMOS33 } [get_ports { LED16_B }]; #IO_L5P_T0_D06_14 Sch=led16_b
8 set_property -dict { PACKAGE_PIN M16 IOSTANDARD LVCMOS33 } [get_ports { LED16_G }]; #IO_L10P_T1_D14_14 Sch=led16_g
9 set_property -dict { PACKAGE_PIN N15 IOSTANDARD LVCMOS33 } [get_ports { LED16_R }]; #IO_L11P_T1_SRCC_14 Sch=led16_r
```



3

# 七段数码管


## ④ 七段LED数码管

### ① 共阳极

NEXYS4 (DDR)



- 点亮，引脚输出为低电平(0)
- 熄灭，引脚输出为高电平(1)

### ② 共阴极

 

AN0..7取反了

 
 
Both the **AN0..7** and the **CA..AG/DP** signals are driven **low** when active.



# 七段数码管-方案1

## 共阳极

- 点亮，引脚输出为低电平(0)
- 熄灭，引脚输出为高电平(1)

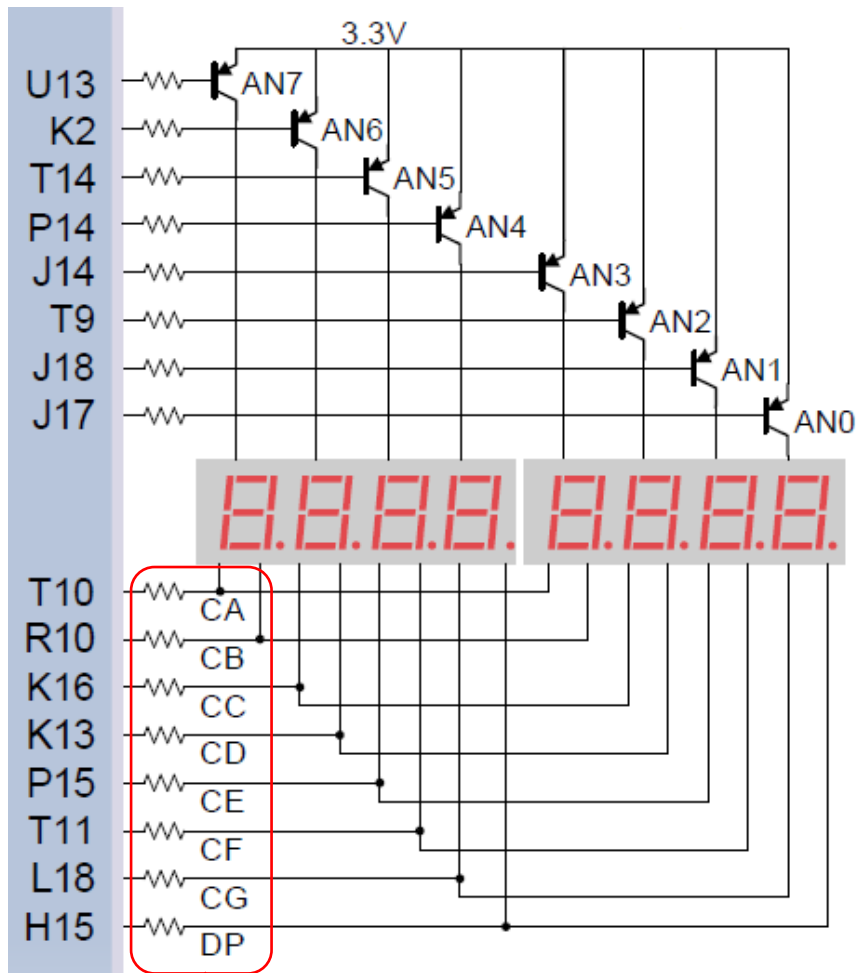 

接到所有的 8

```

1  module SevenSegLED(
2      input  logic [3:0] SW,
3      output logic [3:0] AN,    //使能
4      output logic      DP,    //小数点
5      output logic [6:0] A2G );
6
7      assign AN = 4'b0000; // 右侧4个全亮
8      assign DP = 1;      // DP off
9      // A2G format {a, b, c, d, e, f, g}
10     always_comb
11         case (SW)
12             'h0: A2G = 7'b0000001;
13             'h1: A2G = 7'b1001111;
14             'h2: A2G = 7'b0010010;
15             'h3: A2G = 7'b0000110;
16             'h4: A2G = 7'b1001100;
17             'h5: A2G = 7'b0100100;
18             'h6: A2G = 7'b0100000;
19             'h7: A2G = 7'b0001111;
20             'h8: A2G = 7'b0000000;
21             'h9: A2G = 7'b0000100;
22             'hA: A2G = 7'b0001000;
23             'hB: A2G = 7'b1100000;
24             'hC: A2G = 7'b0110001;
25             'hD: A2G = 7'b1000010;
26             'hE: A2G = 7'b0110000;
27             'hF: A2G = 7'b0111000;
28             default: A2G = 7'b0000001; //0
29         endcase
30 endmodule

```

## 7SegmentLED

# 七段数码管-方案1



都显示同一个数字？

```
1 module SevenSegLED(  
2     input  logic [3:0] SW,  
3     output logic [3:0] AN,    //使能  
4     output logic      DP,    //小数点  
5     output logic [6:0] A2G );  
6  
7     assign AN = 4'b0000; // 右侧4个全亮  
8     assign DP = 1;       // DP off  
9     // A2G format {a, b, c, d, e, f, g}  
10    always_comb  
11        case (SW)  
12            'h0: A2G = 7'b0000001;  
13            'h1: A2G = 7'b1001111;  
14            'h2: A2G = 7'b0010010;  
15            'h3: A2G = 7'b0000110;  
16            'h4: A2G = 7'b1001100;  
17            'h5: A2G = 7'b0100100;  
18            'h6: A2G = 7'b0100000;  
19            'h7: A2G = 7'b0001111;  
20            'h8: A2G = 7'b0000000;  
21            'h9: A2G = 7'b0000100;  
22            'hA: A2G = 7'b0001000;  
23            'hB: A2G = 7'b1100000;  
24            'hC: A2G = 7'b0110001;  
25            'hD: A2G = 7'b1000010;  
26            'hE: A2G = 7'b0110000;  
27            'hF: A2G = 7'b0111000;  
28            default: A2G = 7'b0000001; //0  
29        endcase  
30 endmodule
```

16  
进制七段  
译码器

Nexys4DDR\_Master.xdc

```
1 ##Switches  
2 set_property -dict { PACKAGE_PIN J15 IOSTANDARD LVCMOS33 } [get_ports { SW[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]  
3 set_property -dict { PACKAGE_PIN L16 IOSTANDARD LVCMOS33 } [get_ports { SW[1] }]; #IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]  
4 set_property -dict { PACKAGE_PIN M13 IOSTANDARD LVCMOS33 } [get_ports { SW[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]  
5 set_property -dict { PACKAGE_PIN R15 IOSTANDARD LVCMOS33 } [get_ports { SW[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]  
6  
7 ##7 segment display  
8 set_property -dict { PACKAGE_PIN T10 IOSTANDARD LVCMOS33 } [get_ports { A2G[6] }]; #IO_L24N_T3_A00_D16_14 Sch=ca  
9 set_property -dict { PACKAGE_PIN R10 IOSTANDARD LVCMOS33 } [get_ports { A2G[5] }]; #IO_25_14 Sch=cb  
10 set_property -dict { PACKAGE_PIN K16 IOSTANDARD LVCMOS33 } [get_ports { A2G[4] }]; #IO_25_15 Sch=cc  
11 set_property -dict { PACKAGE_PIN K13 IOSTANDARD LVCMOS33 } [get_ports { A2G[3] }]; #IO_L17P_T2_A26_15 Sch=cd  
12 set_property -dict { PACKAGE_PIN P15 IOSTANDARD LVCMOS33 } [get_ports { A2G[2] }]; #IO_L13P_T2_MRCC_14 Sch=ce  
13 set_property -dict { PACKAGE_PIN T11 IOSTANDARD LVCMOS33 } [get_ports { A2G[1] }]; #IO_L19P_T3_A10_D26_14 Sch=cf  
14 set_property -dict { PACKAGE_PIN L18 IOSTANDARD LVCMOS33 } [get_ports { A2G[0] }]; #IO_L4P_T0_D04_14 Sch=cg  
15 set_property -dict { PACKAGE_PIN H15 IOSTANDARD LVCMOS33 } [get_ports { DP }]; #IO_L19N_T3_A21_VREF_15 Sch=dp  
16 set_property -dict { PACKAGE_PIN J17 IOSTANDARD LVCMOS33 } [get_ports { AN[0] }]; #IO_L23P_T3_F0E_B_15 Sch=an[0]  
17 set_property -dict { PACKAGE_PIN J18 IOSTANDARD LVCMOS33 } [get_ports { AN[1] }]; #IO_L23N_T3_FWE_B_15 Sch=an[1]  
18 set_property -dict { PACKAGE_PIN T9 IOSTANDARD LVCMOS33 } [get_ports { AN[2] }]; #IO_L24P_T3_A01_D17_14 Sch=an[2]  
19 set_property -dict { PACKAGE_PIN J14 IOSTANDARD LVCMOS33 } [get_ports { AN[3] }]; #IO_L19P_T3_A22_15 Sch=an[3]
```



# 7段数码管 - 方案2

## 顶层文件

```

1 module Hex7Seg_Top(
2     input  logic [3:0]SW,
3     output logic [6:0]A2G,
4     output logic [3:0]AN,
5     output logic DP );
6
7     assign AN = 4'b0000; // 右侧4个亮
8     assign DP = 1;      // all dp off
9
10    // 实例化 7段数码管
11    Hex7Seg S7(.data(SW), .a2g(A2G));
12 endmodule

```




```

1 module Hex7Seg(
2     input  logic [3:0] data,
3     output logic [6:0] a2g );
4
5 // assign AN = 4'b0000; // 右侧4个全亮
6 // assign DP = 1;      // DP off
7
8 // a2g format {a, b, c, d, e, f, g}
9 always_comb
10     case (data)
11         'h0: a2g = 7'b0000001;
12         'h1: a2g = 7'b1001111;
13         'h2: a2g = 7'b0010010;
14         'h3: a2g = 7'b0000110;
15         'h4: a2g = 7'b1001100;
16         'h5: a2g = 7'b0100100;
17         'h6: a2g = 7'b0100000;
18         'h7: a2g = 7'b0001111;
19         'h8: a2g = 7'b0000000;
20         'h9: a2g = 7'b0000100;
21         'hA: a2g = 7'b0001000;
22         'hB: a2g = 7'b1100000;
23         'hC: a2g = 7'b0110001;
24         'hD: a2g = 7'b1000010;
25         'hE: a2g = 7'b0110000;
26         'hF: a2g = 7'b0111000;
27         default: a2g = 7'b0000001; //0
28     endcase
29 endmodule

```


16进制七段译码器

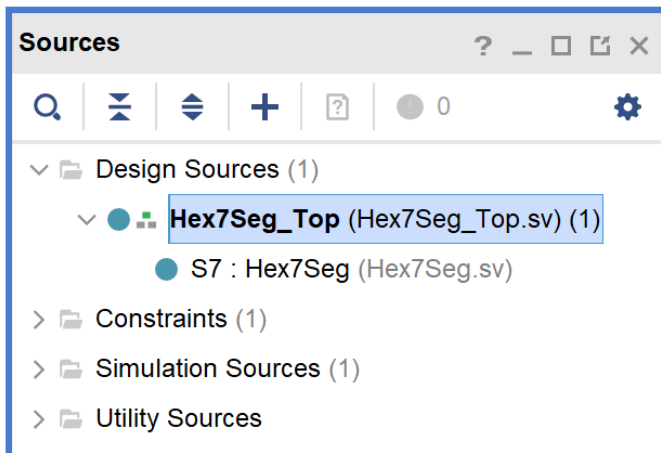

# 七段数码管 - 方案3

```
assign AN = 4'b1101;
```

只显示右侧第2个




 


16  
进制  
七段  
译码  
器

```
1 module SevenSegLED(  
2     input  logic [3:0] SW,  
3     output logic [3:0] AN,    //使能  
4     output logic      DP,    //小数点  
5     output logic [6:0] A2G );  
6  
7     assign AN = 4'b1101; // 只点亮右侧第2个  
8     assign DP = 1;      // DP on  
9     // A2G format {a, b, c, d, e, f, g}  
10    always_comb  
11        case (SW)  
12            'h0: A2G = 7'b0000001;  
13            'h1: A2G = 7'b1001111;  
14            'h2: A2G = 7'b0010010;  
15            'h3: A2G = 7'b0000110;  
16            'h4: A2G = 7'b1001100;  
17            'h5: A2G = 7'b0100100;  
18            'h6: A2G = 7'b0100000;  
19            'h7: A2G = 7'b0001111;  
20            'h8: A2G = 7'b0000000;  
21            'h9: A2G = 7'b0000100;  
22            'hA: A2G = 7'b0001000;  
23            'hB: A2G = 7'b1100000;  
24            'hC: A2G = 7'b0110001;  
25            'hD: A2G = 7'b1000010;  
26            'hE: A2G = 7'b0110000;  
27            'hF: A2G = 7'b0111000;  
28            default: A2G = 7'b0000001; //0  
29        endcase  
30    endmodule
```


mux7seg

# 方案4：复用七段数码管

    

拨码开关控制哪个数码管亮

SW[3]	SW[2]	SW[1]	SW[0]	s[1]	s[0]
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

 

```

1 module mux7seg( input  logic [3:0] SW,
2                 output logic [6:0] A2G,
3                 output logic [3:0] AN,
4                 output logic          DP);
5
6
7     logic [15:0] x;
8     logic [3:0] digit;
9
10    assign x = 'h1234;
11    assign AN = ~SW;
12    assign DP = 1;    // DP off
13
14    logic [1:0] s;
15    assign s[1] = SW[2] | SW[3];
16    assign s[0] = SW[1] | SW[3];
17
18    //4位 4选1 MUX: mux44
19    always_comb
20    case(s)
21        0: digit = x[3:0];
22        1: digit = x[7:4];
23        2: digit = x[11:8];
24        3: digit = x[15:12];
25        default: digit = x[3:0];
26    endcase
27
28    //实例化 7段数码管
29    Hex7Seg s7(.x(digit), .a2g(A2G));
30 endmodule



```




# 手工复用

VS

# 分时复用

  

用clk快速、反复代替SW[3:0]

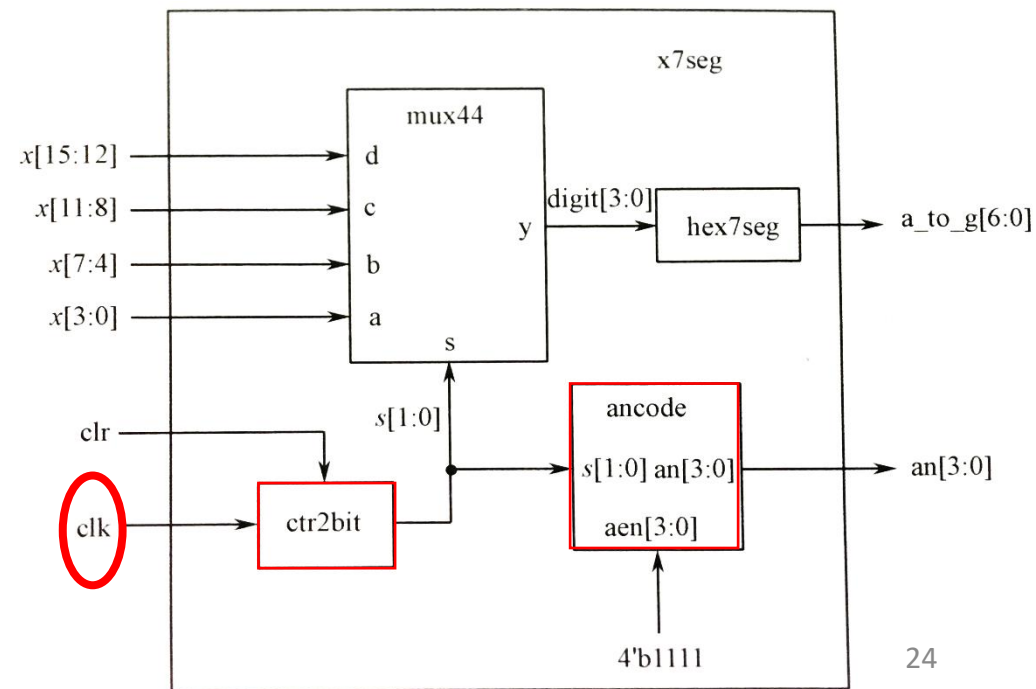




## 方案5：分时显示

```

1 module x7seg( input logic [15:0] data,
2               input logic      clk,
3               input logic      clr,
4               output logic [6:0] a2g,
5               output logic [3:0] an, //数码管使能
6               output logic      dp ); //小数点

```

 

4个七段数码管分别显示，  
每个数字每秒刷新190次

```

8   logic [1:0] s;      //选择哪个数码管
9   logic [3:0] digit;
10  logic [19:0] clkdiv;

```

```

12  assign dp = 1;      // DP off
13  assign s = clkdiv[19:18]; // 190Hz


```

//4个数码管 4选1 (MUX44)

```

16  always_comb
17  case(s)
18      0: digit = data[3:0];
19      1: digit = data[7:4];
20      2: digit = data[11:8];
21      3: digit = data[15:12];
22      default: digit = data[3:0];
23  endcase

```

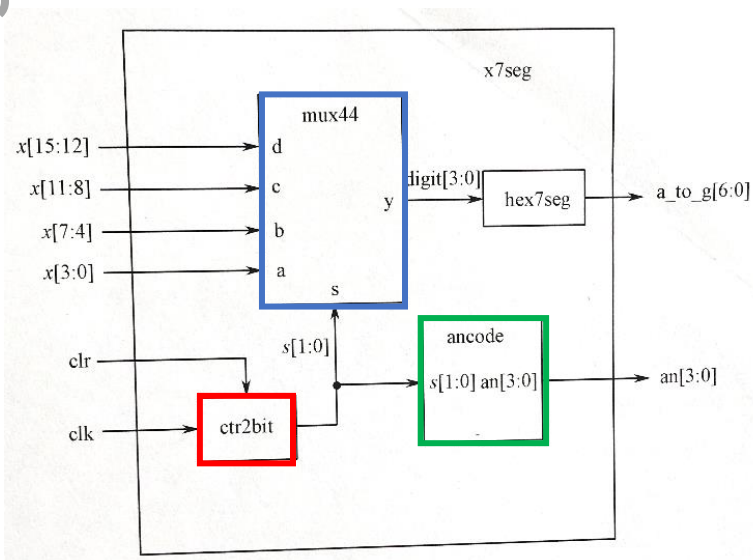

//4个数码管的使能

```

25  always_comb
26  case(s)
27      0: an = 4'b1110;
28      1: an = 4'b1101;
29      2: an = 4'b1011;
30      3: an = 4'b0111;
31      default: an = 4'b1110;
32  endcase

```

// 时钟分频器 (20位二进制计数器)

```

35  always @(posedge clk, posedge clr)
36  if(clr == 1) clkdiv <= 0;
37  else
38      clkdiv <= clkdiv + 1;
39
40  //实例化 7段数码管
41  Hex7Seg H7(.digit(digit), .a2g(a2g));
42  endmodule

```

## 方案5：分时显示

顶层文件

```


1 module x7seg( input logic [15:0] data,
2               input logic      clk,
3               input logic      clr,
4               output logic [6:0] a2g,
5               output logic [3:0] an, //数码管使能
6               output logic      dp ); //小数点
7
8   logic [1:0] s;    //选择哪个数码管
9   logic [3:0] digit;
10  logic [19:0] clkdiv;
11
12  assign dp = 1;    // DP off
13  assign s = clkdiv[19:18]; // count every 10.4ms
14
15  //4个数码管 4选1 (MUX44)
16  always_comb
17  case(s)
18    0: digit = data[3:0];
19    1: digit = data[7:4];
20    2: digit = data[11:8];
21    3: digit = data[15:12];
22    default: digit = data[3:0];
23  endcase

```

```

1 module x7seg_Top(
2     input logic      CLK100MHZ,
3     input logic [0:0] SW,
4     output logic [6:0] A2G,
5     output logic [3:0] AN,
6     output logic      DP );
7
8     logic [15:0] x;
9     assign x = 'h1234; //test value
10
11     x7seg X7(.data(x),
12              .clk (CLK100MHZ),
13              .clr (SW[0]),
14              .a2g (A2G),
15              .an  (AN),
16              .dp  (DP) );
17 endmodule

```

 


# 方案5：分时显示

## 约束文件

```

1  ## Clock signal
2  set_property -dict { PACKAGE_PIN E3      IOSTANDARD LVCMOS33 } [get_ports { CLK100MHZ }]; #IO_L12P_T1_MRCC_35 Sch=clk100mhz
3  create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports {CLK100MHZ}];
4
5  ##Switches
6  set_property -dict { PACKAGE_PIN J15      IOSTANDARD LVCMOS33 } [get_ports { SW[0] }]; #IO_L24N_T3_RS0_15 Sch=sw[0]
7  #set_property -dict { PACKAGE_PIN L16      IOSTANDARD LVCMOS33 } [get_ports { SW[1] }]; #IO_L3N_T0_DQS_EMCCLK_14 Sch=sw[1]
8  #set_property -dict { PACKAGE_PIN M13      IOSTANDARD LVCMOS33 } [get_ports { SW[2] }]; #IO_L6N_T0_D08_VREF_14 Sch=sw[2]
9  #set_property -dict { PACKAGE_PIN R15      IOSTANDARD LVCMOS33 } [get_ports { SW[3] }]; #IO_L13N_T2_MRCC_14 Sch=sw[3]
10
11 ##7 segment display
12 set_property -dict { PACKAGE_PIN T10      IOSTANDARD LVCMOS33 } [get_ports { A2G[0] }]; #IO_L24N_T3_A00_D16_14 Sch=ca
13 set_property -dict { PACKAGE_PIN R10      IOSTANDARD LVCMOS33 } [get_ports { A2G[1] }]; #IO_25_14 Sch=cb
14 set_property -dict { PACKAGE_PIN K16      IOSTANDARD LVCMOS33 } [get_ports { A2G[2] }]; #IO_25_15 Sch=cc
15 set_property -dict { PACKAGE_PIN K13      IOSTANDARD LVCMOS33 } [get_ports { A2G[3] }]; #IO_L17P_T2_A26_15 Sch=cd
16 set_property -dict { PACKAGE_PIN P15      IOSTANDARD LVCMOS33 } [get_ports { A2G[4] }]; #IO_L13P_T2_MRCC_14 Sch=ce
17 set_property -dict { PACKAGE_PIN T11      IOSTANDARD LVCMOS33 } [get_ports { A2G[5] }]; #IO_L19P_T3_A10_D26_14 Sch=cf
18 set_property -dict { PACKAGE_PIN L18      IOSTANDARD LVCMOS33 } [get_ports { A2G[6] }]; #IO_L4P_T0_D04_14 Sch=cg
19 set_property -dict { PACKAGE_PIN H15      IOSTANDARD LVCMOS33 } [get_ports { DP }]; #IO_L19N_T3_A21_VREF_15 Sch=dp
20 set_property -dict { PACKAGE_PIN J17      IOSTANDARD LVCMOS33 } [get_ports { AN[0] }]; #IO_L17P_T2_A26_15 Sch=ad
21 set_property -dict { PACKAGE_PIN J18      IOSTANDARD LVCMOS33 } [get_ports { AN[1] }]; #IO_L18P_T3_A11_D27_14 Sch=ae
22 set_property -dict { PACKAGE_PIN T9       IOSTANDARD LVCMOS33 } [get_ports { AN[2] }]; #IO_L16P_T2_A25_15 Sch=af
23 set_property -dict { PACKAGE_PIN J14      IOSTANDARD LVCMOS33 } [get_ports { AN[3] }]; #IO_L17P_T2_A26_15 Sch=ag
24 set_property -dict { PACKAGE_PIN P14      IOSTANDARD LVCMOS33 } [get_ports { AN[4] }]; #IO_L13P_T2_MRCC_14 Sch=ah
25 set_property -dict { PACKAGE_PIN T14      IOSTANDARD LVCMOS33 } [get_ports { AN[5] }]; #IO_L19P_T3_A10_D26_14 Sch=ai
26 set_property -dict { PACKAGE_PIN K2       IOSTANDARD LVCMOS33 } [get_ports { AN[6] }]; #IO_L17P_T2_A26_15 Sch=aj
27 set_property -dict { PACKAGE_PIN U13      IOSTANDARD LVCMOS33 } [get_ports { AN[7] }]; #IO_L23N_T3_A02_D18_14 Sch=an[7]

```

 

```


1  module x7seg_Top(
2      input logic CLK100MHZ,
      input logic [0:0] SW,
      output logic [6:0] A2G,
      output logic [3:0] AN,
      output logic      DP );

      logic [15:0] x;
      assign x = 'h1234; //test value


      x7seg X7(.data(x),
               .clk (CLK100MHZ),
               .clr (SW[0]),
               .a2g (A2G),
               .an  (AN),
               .dp  (DP) );
endmodule

```

# 方案5：分时显示

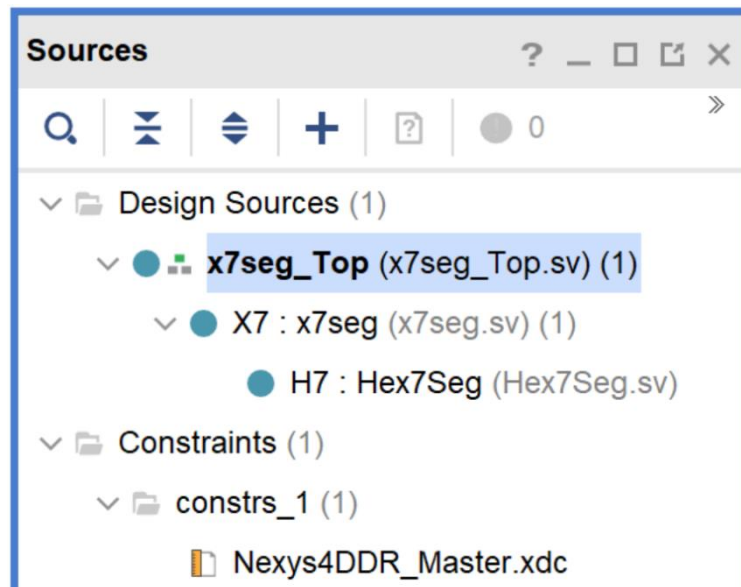

Top 与板子相连

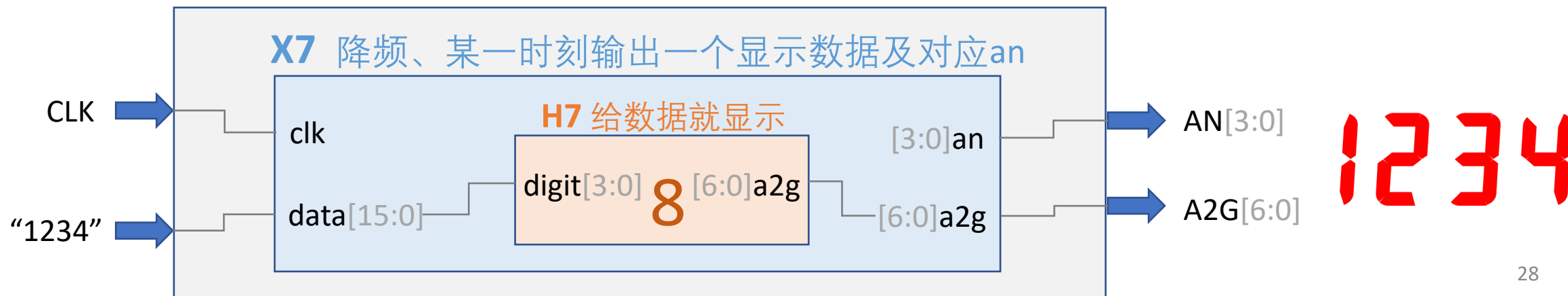



# 时钟分频器

q(i)	频率 Hz	周期 ms	q(i)	频率 Hz	周期 ms
In	100M	0.000 01	12	12 207.03	0.081 92
0	50M	0.000 02	13	6 103.52	0.163 84
1	25M	0.000 04	14	3 051.76	0.327 68
2	12.5M	0.000 08	15	1 525.88	0.655 36
3	6.25M	0.000 16	16	762.94	1.310 72
4	3.125M	0.000 32	17	381.47	2.621 44
5	1.5625M	0.000 64	18	190.73	5.242 88
6	781.25K	0.001 28	19	95.37	10.485 76
7	390.625K	0.002 56	20	47.68	20.010 24
8	195.3125K	0.005 12	21	23.84	41.943 04
9	97 656.25	0.010 24	22	11.92	83.886 08
10	48 828.13	0.020 48	23	5.96	167.772 16
11	24 414.06	0.040 96	24	2.98	335.544 32

```
1 module clkdiv(  
2     input mclk,  
3     input clr,  
4     output clk190, //190Hz  
5     output clk48); // 48Hz  
6  
7     reg [24:0] q; //25位计数器  
8  
9     always @(posedge mclk or posedge clr)  
10    begin  
11        if(clr==1)  
12            q <= 0;  
13        else  
14            q <= q + 1;  
15        end  
16  
17        assign clk190 = q[18];  
18        assign clk48 = q[20];  
19    endmodule
```




# 闪烁的LED

q(i)	频率 Hz	周期 ms	q(i)	频率 Hz	周期 ms
In	100M	0.000 01	12	12 207.03	0.081 92
0	50M	0.000 02	13	6 103.52	0.163 84
1	25M	0.000 04	14	3 051.76	0.327 68
2	12.5M	0.000 08	15	1 525.88	0.655 36
3	6.25M	0.000 16	16	762.94	1.310 72
4	3.125M	0.000 32	17	381.47	2.621 44
5	1.5625M	0.000 64	18	190.73	5.242 88
6	781.25K	0.001 28	19	95.37	10.485 76
7	390.625K	0.002 56	20	47.68	20.010 24
8	195.3125K	0.005 12	21	23.84	41.943 04
9	97 656.25	0.010 24	22	11.92	83.886 08
10	48 828.13	0.020 48	23	5.96	167.772 16
11	24 414.06	0.040 96	24	2.98	335.544 32

```

1 module blinkLED(
2     input logic CLK100MHZ,
3     output logic [1:0] LED );
4
5     logic [30:0] blinkCount;
6
7     always @(posedge CLK100MHZ)
8         blinkCount <= blinkCount + 1;
9
10    assign LED[0] = blinkCount[25]; //Slow
11    assign LED[1] = blinkCount[24]; //Fast
12 endmodule

```

 

# 参考资料



- Nexys4-DDR\_Reference Manual.pdf



- Nexys4-DDR\_sch.PDF



- lab1 Vivado Design Flow.pdf



- lab1 Vivado Design Flow.zip

引脚约束文件

- Nexys4DDR\_Master.xdc

<https://www.xilinx.com/>

<https://china.xilinx.com/>

# \*扩展模块 PmodKYPD

*a 16 button keypad*


## Decoder Behavior

The Decoder determines which key, if any, was pressed on the PmodKYPD by cycling through each column pin with a logic low. After the Decoder sets a **column pin low**, it checks for a **logic low in the row pins**. A low in a row pin signifies that a button has been pressed. Once the Decoder has both the row and column of the key, it can determine the corresponding **value** to output to the **DisplayController**. The decoder will change columns every **1ms** in its cycle.


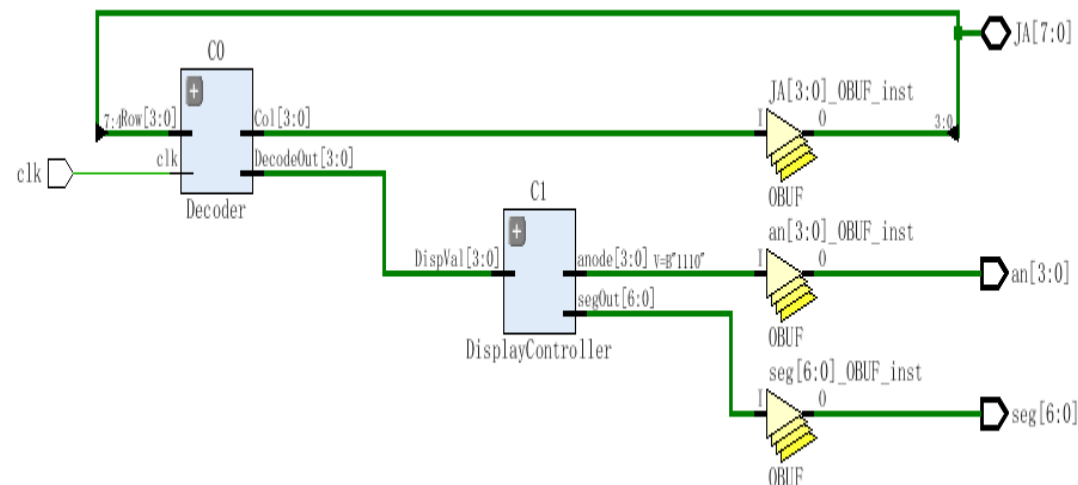
## DisplayController Behavior

The DisplayController is used to display the output of the Decoder onto the seven segment display on a Nexys4 board. In this project only the rightmost digit on the seven segment display is used. Before any key was pressed, the seven segment display shows a '0' on the rightmost digit. The keypad is represented in hex values.



# \* USB Keyboard

## 1) Initial state

Initially, the 7 segment display will show all 0's.

## 2) Key Press

When a button is pressed, the value of the scan code will shift onto the 7 segment display. In the picture, 'a' is pressed, so a scan code of "1C" is displayed.

## 3) Key Release

When the 'a' key is released, a scan code of "F01C" is shifted onto the 7 segment display. The initial scan code of "1C" is shifted to the left display.

## 4) Multi key press

When multiple keys are pressed their scan codes are shifted in order. In this case, Q ("15") was pressed, followed by W ("1D").



ESC 76	F1 05	F2 06	F3 04	F4 0C	F5 03	F6 0B	F7 83	F8 0A	F9 01	F10 09	F11 78	F12 07	
`~ 0E	1! 16	2@ 1E	3# 26	4\$ 25	5% 2E	6^ 36	7& 3D	8* 3E	9( 46	0) 45	-_ 4E	=+ 55	BackSpace ← 66
TAB 0D	Q 15	W 1D	E 24	R 2D	T 2C	Y 35	U 3C	I 43	O 44	P 4D	[{ 54	]} 5B	\  5D
Caps Lock 58	A 1C	S 1B	D 23	F 2B	G 34	H 33	J 3B	K 42	L 4B	:: 4C	"" 52	Enter ↵ 5A	
Shift 12	Z 1Z	X 22	C 21	V 2A	B 32	N 31	M 3A	,< 41	>. 49	/? 4A	↑ 59		Shift 59
Ctrl 14	Alt 11	Space 29								Alt E0 11	Ctrl E0 14		

Figure 9. Keyboard scan codes.